

# CZ1005 Digital Logic AS1819 sem1

Name: Wu Sibing Email: WUSI0008@e.ntu.edu.sg

$$1. (a) \quad (i) \quad \begin{array}{r} 16 \overline{) 98765} \quad 13 \\ 16 \overline{) 6172} \quad 12 \\ 16 \overline{) 385} \quad 1 \\ 16 \overline{) 24} \quad 8 \\ 16 \overline{) 1} \quad 0 \end{array}$$

$$\therefore 181CD_{16}$$

$$(ii) \quad 16 \overline{) 98} \quad 2$$

$$\therefore 98 = 62_{16}$$

$$\therefore 62.C3_{16}$$

$$0.765 \times 16 = 12.24$$

$$0.24 \times 16 = 3.84$$

$$\therefore C3_{16}$$

$$(b) \quad 3 = 11_2 \quad 2 \text{ digits}$$

$$2^{-m} < 0.141592$$

$$m > \log_{0.5} 0.141592 = 2.82$$

$$\therefore m \geq 3$$

$$\therefore \text{need } 2+3 = 5 \text{ bits}$$

(c)

$$\begin{aligned} & \{[(A'+C')(B'C'D)'][(A'+B)'+C']D'\}' \\ &= (A'+C')(B'C'D)' + [(A'+B)'+C'] + D \\ &= (A'+C')(B+C+D') + (A'+B)C + D \\ &= \underline{A'B} + \underline{A'C} + \underline{A'D'} + \underline{BC'} + \underline{C'D'} + \underline{A'C} + \underline{BC} + D \\ &= \underline{A'B} + \underline{A'C} + \underline{A'D'} + \underline{C'D'} + \underline{B} + D \\ &= \underline{A'C} + \underline{A'D'} + \underline{C'D'} + \underline{B} + D \\ &= \underline{CA'} + \underline{C'D'} + \underline{A'D'} + \underline{B} + D \\ &= \underline{CA'} + \underline{C'D'} + \underline{B} + \underline{D} \\ &= \underline{CA'} + \underline{C'} \quad B + D \quad \downarrow (A+A'B = A+B) \\ &= \underline{A'} \quad B + \underline{C'} + D \end{aligned}$$

(d)


$$0101011 = 1 \times 2^6 + 1 \times 2^4 + 1 \times 2^2 + 1 \times 2^1 + 1 \times 2^0 = 87$$

$$11100110 = -(1 \times 2^6 + 1 \times 2^5 + 1 \times 2^2 + 1 \times 2^1) = -102$$

$$00110011 = 1 \times 2^5 + 1 \times 2^4 + 1 \times 2^1 + 1 \times 2^0 = 51$$

$$11101001 = -(00010111) \\ = -(1 \times 2^4 + 1 \times 2^2 + 1 \times 2^1 + 1 \times 2^0) = -23$$
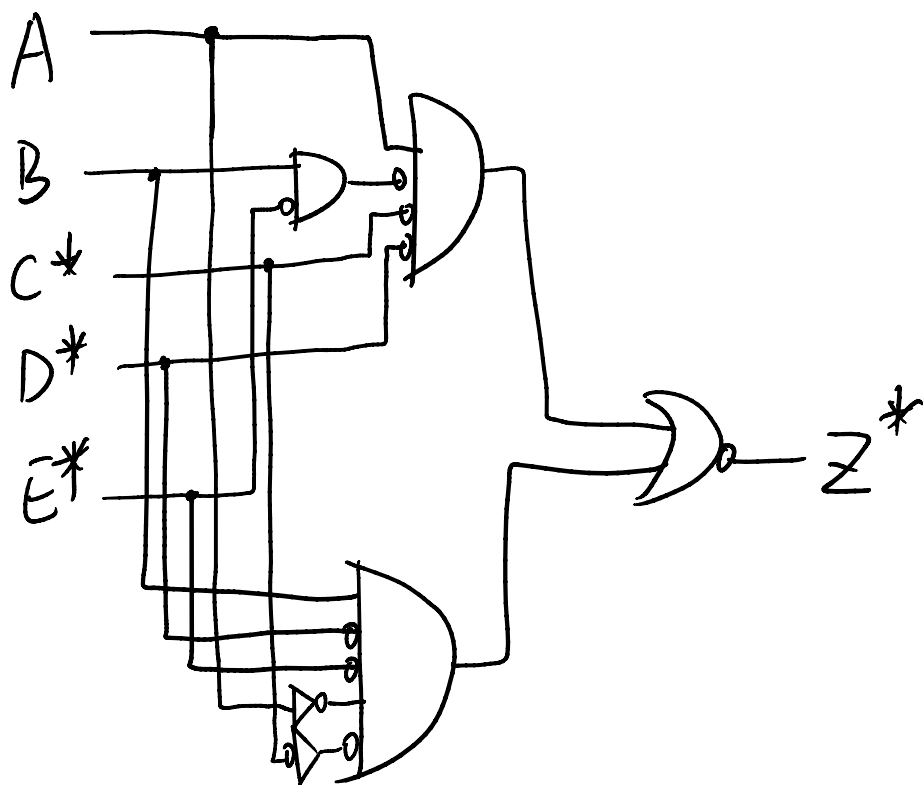
$$(e) Z^* = [A' + C^* + D^* + B(E^*)'] [B' + D^* + \bar{E}^* + A + (C^*)']$$



2.

(a)  $-7: 0111 \xrightarrow{\text{2's complement}} 1001$

$-6: 0110 \xrightarrow{\text{2's complement}} 1010$

$1001 \rightarrow -7$

$\times 1010 \rightarrow -6$

$00000000$




$1111001$


$000000$

$0,0,1,1,1 \xrightarrow{\text{2's complement}}$

$00101010 \rightarrow 42$

(b) use Schmitt-trigger buffer

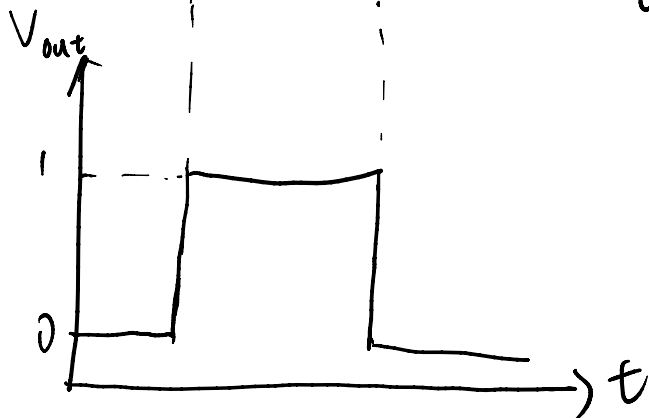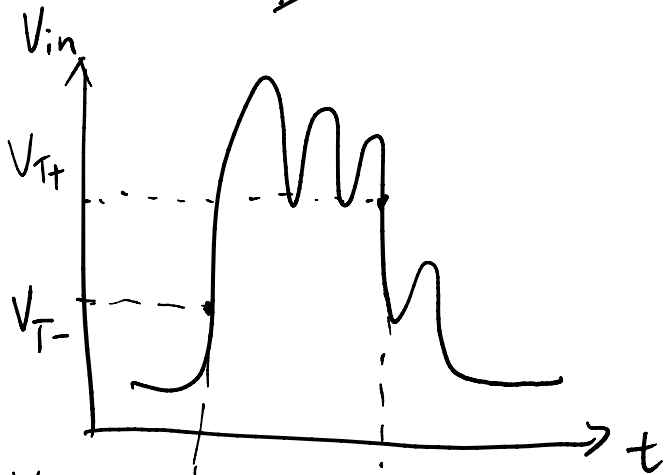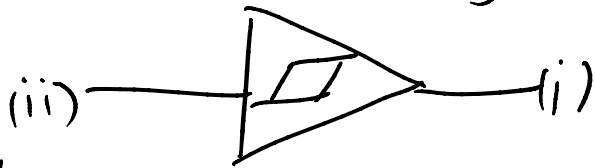


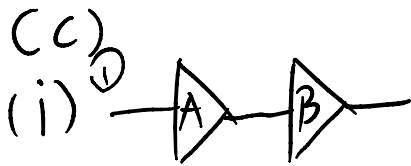

If  $V_{OH}(\min)(A) \geq V_{IH}(\min)(B)$ ,  $V_{OL}(\max)(A) \leq V_{IL}(\max)(B)$ ,  
 $I_{OH}(\max)(A) \geq I_{IH}(\max)(B)$ ,  $I_{OL}(\max)(A) \geq I_{IL}(\max)(B)$ , then A drives B.

$V_{OH}(\min)(A) = 3.3V$ ,  $V_{IH}(\min)(B) = 3.5V$ ,  $V_{OH}(\min)(A) < V_{IH}(\max)(B)$ ;

Hence A does not drive B.

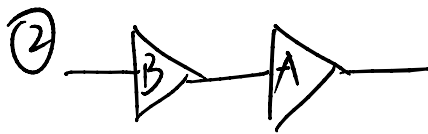

If  $V_{OH}(\min)(B) \geq V_{IH}(\min)(A)$ ,  $V_{OL}(\max)(B) \leq V_{IL}(\max)(A)$ ,  
 $I_{OH}(\max)(B) \geq I_{IH}(\max)(A)$ ,  $I_{OL}(\max)(B) \geq I_{IL}(\max)(A)$ , then B drives A.

$V_{OH}(\min)(B) = 4.5V$ ,  $V_{IH}(\min)(A) = 2.0V$ ,  $V_{OH}(\min)(B) > V_{IH}(\max)(A)$ ;

$V_{OL}(\max)(B) = 0.6V$ ,  $V_{IL}(\max)(A) = 0.8V$ ,  $V_{OL}(\max)(B) < V_{IL}(\max)(A)$ ;

$I_{OH}(\max)(B) = 19mA$ ,  $I_{IH}(\max)(A) = 0.6mA$ ,  $I_{OH}(\max)(B) > I_{IH}(\max)(A)$ ;

$I_{OL}(\max)(B) = 21mA$ ,  $I_{IL}(\max)(A) = 0.8mA$ ,  $I_{OL}(\max)(A) > I_{IL}(\max)(B)$ ;

Hence B drives A.

(ii)

$$\text{fan-out} = \min \left\{ \frac{I_{OH}}{I_{IH}}, \frac{I_{OL}}{I_{IL}} \right\}$$

$$= \min \left\{ \frac{19}{0.6}, \frac{21}{0.8} \right\}$$

$$= 26.25 = 26$$

Fan-out has to be an integer since it specifies the number of standard loads that the output gate can drive

(d)  $V=0$

ab		c	
		0	1
0	0	1	1
0	1	0	1
1	1	0	x
1	0	0	1

$V=1$


ab		c	
		0	1
0	0	1	0
0	1	0	0
1	1	0	x
1	0	1	1

$$V'(a'b' + c) + V(b'c' + ac)$$

$$= V'a'b' + V'c + Vb'c' + Vac$$

3 (a)

(i)

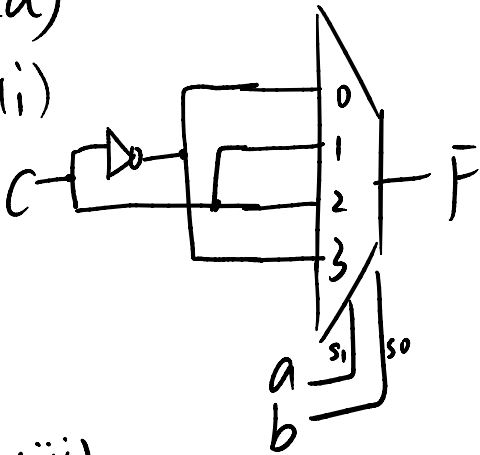

(ii)

ab		c	
		0	1
0	0	1	0
0	1	0	1
1	1	1	0
1	0	0	1

$$F = a'b'c' + ab'c + a'bc + abc'$$

(iii)

**module** simplecircuit (**input** a,b,c, **output** F);

**assign** F = (~a & ~b & ~c) | (a & ~b & c) | (~a & b & c) | (a & b & ~c);

**endmodule**

(b)

**module** decoder2\_4 (**input** [1:0] Cin, **output reg** [3:0] Cout);

**always** @ \*

**case**(Cin)

2'b00 : Cout = 4'b0001;

2'b01 : Cout = 4'b0010;


2'b10 : Cout = 4'b0100;

2'b11 : Cout = 4'b1000;

**endcase**

**endmodule**

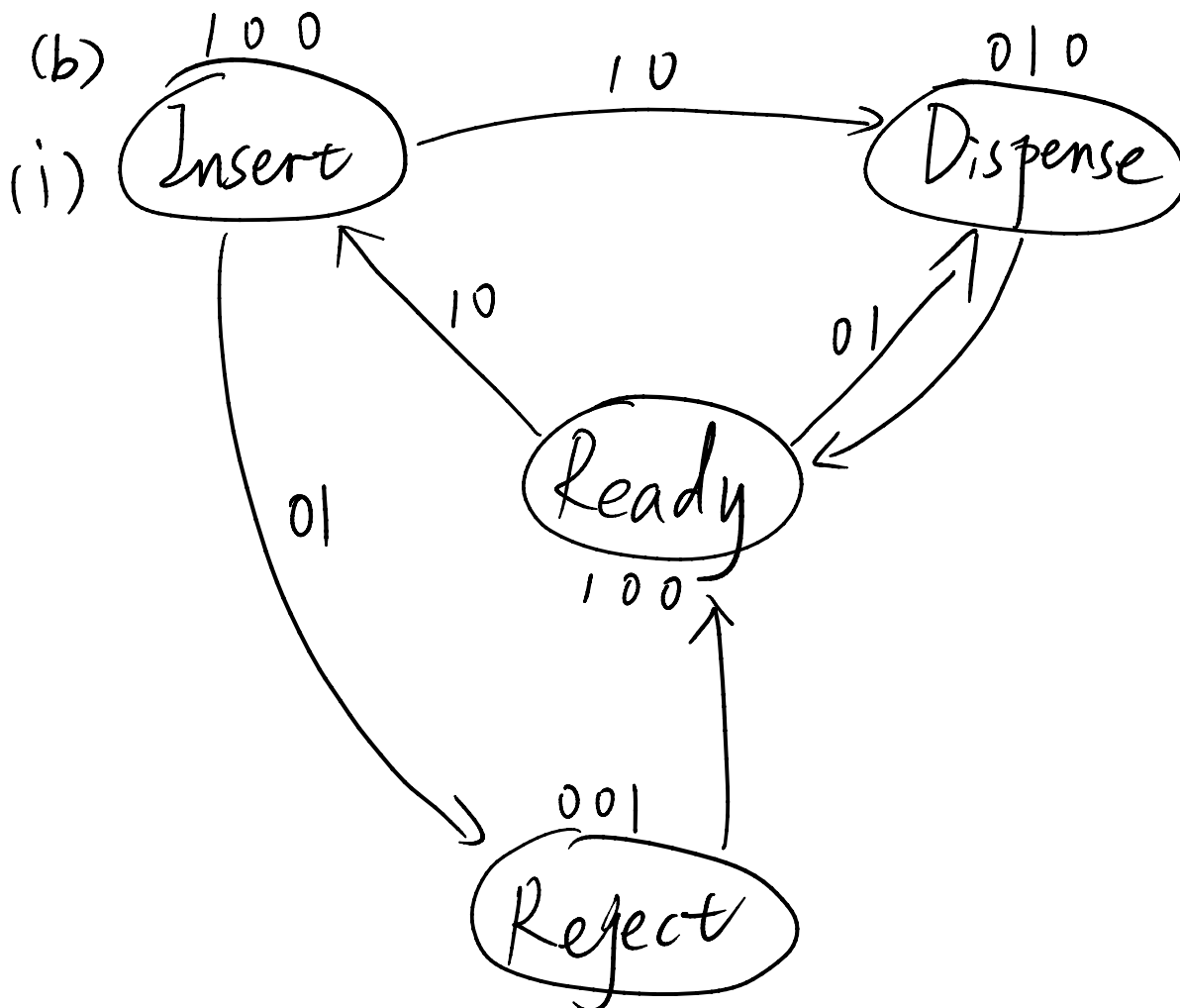4. (a) **module** simplecounter(#parameter WIDTH = 8)  
 (input clk, rst, up, **output reg** [WIDTH-1:0] q);  
**always@(posedge clk)**  
**begin**  
   **if**(rst) q <= 8'b0000\_0000;  
   **else**  
     **if**(up) q <= q + 1'b1;  
     **else** q <= q - 1'b1;  
**end**  
**endmodule**



input: fifty, dollar

output: insert-coin, dispense, reject-money

```
(i) ) module vendor (input clk, rst, fifty, dollar, output reg insert_coin, dispense, reject_money);
```

```
parameter Ready = 2'b00, Insert = 1, Dispense = 2, Reject = 3;  
reg [1:0] st, nst;
```

```
always@(posedge clk or negedge rst)
```

```
begin
```

```
    if(!rst) st <= Ready;
```

```
    else st <= nst;
```

```
end
```

```
always@* begin
```

```
    nst = st;
```

```
    {insert_coin, dispense, reject_money} = 3'b100;
```

```
    case(st)
```

```
        Ready: begin
```

```
            if({fifty, dollar} == 2'b10) nst = Insert;
```

```
            else if ({fifty, dollar} == 2'b01) nst = Dispense;
```

```
            {insert_coin, dispense, reject_money} = 3'b100;
```

```
            end
```

```
        Insert: begin
```

```
            if({fifty, dollar} == 2'b01) nst = Reject;
```

```
            else if ({fifty, dollar} == 2'b10) nst = Dispense;
```

```
            {insert_coin, dispense, reject_money} = 3'b100;
```

```
            end
```

```
        Dispense: begin
```

```
            nst = Ready;
```

```
            {insert_coin, dispense, reject_money} = 3'b010;
```

```
        end
```

Reject: **begin**

nst = Ready;

{insert\_coin, dispense, reject\_money} = 3'b001;

**end**

Default: nst = Ready;

**endcase**

**end**

**endmodule**