

Solver: Jesslyn Chew

- 1 a) It is not memoryless as the output at time t_0 , $y(t_0)$, depends on input other than $t = t_0$ such as $t = t_0 - 2$ and $t = 3 - t_0$.

It is not causal as the output at time t_0 , $y(t_0)$, does not only depend on input for $t \leq t_0$. At $t_0 = 0$, $x(3 - t_0) = x(3)$. This indicates that the input depends 3 seconds before the current time. Hence, it is not causal as it depends on future information.

b)

$$\begin{aligned}
 h(t) &= u(t) - u(t - 4) \\
 x(t) &= e^{-2t}u(t) \\
 y(t) &= \int_{-\infty}^{\infty} h(\tau)x(t - \tau) d\tau \\
 &= \int_{-\infty}^{\infty} (u(\tau) - u(\tau - 4))e^{-2(t-\tau)}u(t - \tau) d\tau \\
 &= \int_{-\infty}^{\infty} u(\tau)e^{-2(t-\tau)}u(t - \tau) d\tau - \int_{-\infty}^{\infty} u(\tau - 4)e^{-2(t-\tau)}u(t - \tau) d\tau \\
 &= \int_0^t e^{-2t+2\tau} d\tau - \int_4^t e^{-2t+2\tau} d\tau \\
 &= e^{-2t} \left(\frac{1}{2} e^{2\tau} \Big|_0^t - \frac{1}{2} e^{2\tau} \Big|_4^t \right) \\
 &= e^{-2t} \left(\frac{1}{2} e^{2t} u(t) - \frac{1}{2} u(t) - \frac{1}{2} e^{2t} u(t - 4) + \frac{1}{2} e^8 u(t - 4) \right) \\
 &= \frac{1}{2} u(t) - \frac{1}{2} e^{-2t} u(t) - \frac{1}{2} u(t - 4) + \frac{1}{2} e^{8-2t} u(t - 4)
 \end{aligned}$$

c)

$$\begin{aligned}
 h(t) &= e^{-2t}u(t) \\
 x(t) &= u(t) - u(t - 4) \\
 H(s) &= \frac{1}{s + 2} \\
 X(s) &= \frac{1}{s} - e^{-4s} \left(\frac{1}{s} \right) \\
 Y(s) &= H(s)X(s) \\
 &= \frac{1}{s(s + 2)} (1 - e^{-4s}) \\
 \frac{1}{s(s + 2)} &= \frac{k_1}{s} + \frac{k_2}{s + 2} \\
 k_1 &= \left[s \cdot \frac{1}{s(s + 2)} \right]_{s=0} = \frac{1}{2} \\
 k_2 &= \left[(s + 2) \cdot \frac{1}{s(s + 2)} \right]_{s=-2} = -\frac{1}{2} \\
 Y(s) &= \left(\frac{1}{2s} - \frac{1}{2(s + 2)} \right) (1 - e^{-4s}) \\
 &= \frac{1}{2} u(t) - \frac{1}{2} e^{-2t} u(t) - \frac{1}{2} u(t - 4) + \frac{1}{2} e^{8-2t} u(t - 4)
 \end{aligned}$$

- 2 a) $x(t) = x(t + T)$ for all t . T is a constant and must be more than 0.

b)

$$\begin{aligned}
 Z_{in} &= \infty \\
 Z_{out} &= 0 \\
 A_0 &= \infty
 \end{aligned}$$

c) i] Yes, there is negative feedback, R_3 provides the negative feedback.

ii] Using superposition, first consider only V_1 and set $V_2 = 0$

$$V_{IN} = \frac{R_1}{R_1 + R_2} V_1$$

$$A_v = 1 + \frac{R_3}{R_4} = \frac{R_3 + R_4}{R_4}$$

$$V_{OUT} = \left(\frac{R_3 + R_4}{R_4} \right) \left(\frac{R_1}{R_1 + R_2} \right) V_1$$

Then, consider only V_2 and set $V_1 = 0$

$$V_{IN} = V_2$$

$$A_v = -\frac{R_3}{R_4}$$

$$V_{OUT} = -\frac{R_3}{R_4} V_2$$

$$\therefore V_{OUT} = \left(\frac{R_3 + R_4}{R_4} \right) \left(\frac{R_1}{R_1 + R_2} \right) V_1 - \frac{R_3}{R_4} V_2$$

- iii]
- (1) Inverting amplifier – $V_1 = 0$
 - (2) Non-inverting amplifier – $V_2 = 0$
 - (3) Unity gain amplifier – $V_2 = 0$, $R_3 = 0$, $R_4 = \infty$