

CE2004 – Circuit and Signal Analysis

Semester 2 Examination 2017-18

Solver : Wilbert

Email : wilb0002@e.ntu.edu.sg

1. (a) Use nodal analysis and take D as the reference point.

No. of equations to be derived =  $4 - 1 = 3$ .

$$V_A = 12V \quad (1)$$

$$V_B = 6V \quad (2)$$

Applying KCL at node C:

Sum of currents entering node C = 0

$$\frac{V_B - V_C}{2k} + \frac{V_A - V_C}{8k} + \frac{V_D - V_C}{4k} = 0 \quad (3)$$

Substitute (1) and (2) into (3),

$$\frac{6 - V_C}{2k} + \frac{12 - V_C}{8k} + \frac{(-V_C)}{4k} = 0$$


$$4(6 - V_C) + (12 - V_C) - 2V_C = 0$$

$$7V_C = 36$$

$$V_C = \frac{36}{7}V$$


$$I_0 = \frac{V_C}{4k} = \frac{36/7}{4k} = \frac{9}{7}mA$$

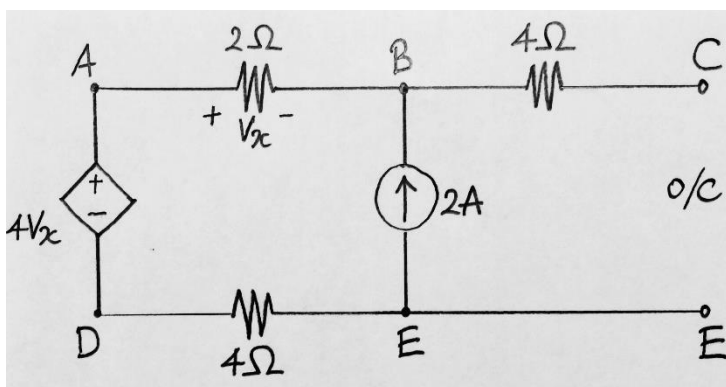- (b) To find  $R_{TH}$  we need to find the voltage across resistor  $R_L$  open-circuit and the current flowing through  $R_L$  short-circuit.



$$\begin{aligned} V_{CE}(o/c) &= V_{BE} & (V_C = V_B \text{ since no current flows from B to C}) \\ &= V_{BA} + V_{AD} + V_{DE} \\ &= (2A)(2\Omega) + 4V_x + (2A)(4\Omega) \\ &= 4 + 4(-2)(2) + 8 \\ &= -4V \end{aligned}$$

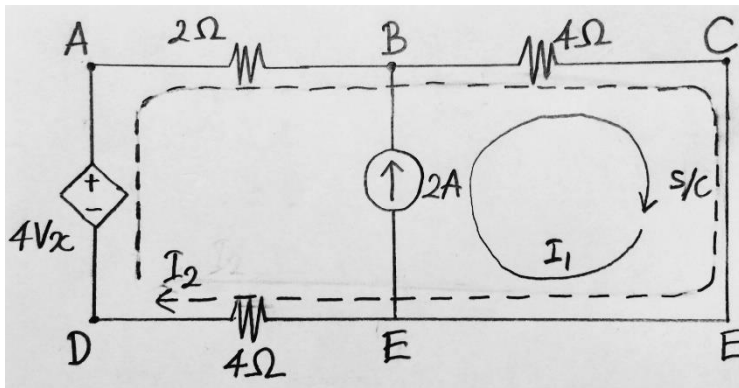Use loop analysis to find  $I_{CE}(s/c)$ .



For Loop 1:  $I_1 = 2A$

For Loop 2:  $(2\Omega)I_2 + (4\Omega)(I_1 + I_2) + (4\Omega)I_2 - 4V_x = 0$

$$2I_2 + 8 + 4I_2 + 4I_2 - 4(2I_2) = 0$$

$$2I_2 = -8$$

$$I_2 = -4A$$

$$I_{CE}(s/c) = I_1 + I_2$$

$$= 2 + (-4)$$


$$= -2A$$

$$R_{TH} = \frac{V_{CE}(o/c)}{I_{CE}(s/c)}$$

$$= \frac{-4}{-2}$$

$$= 2\Omega$$

Thevenin's equivalent circuit:

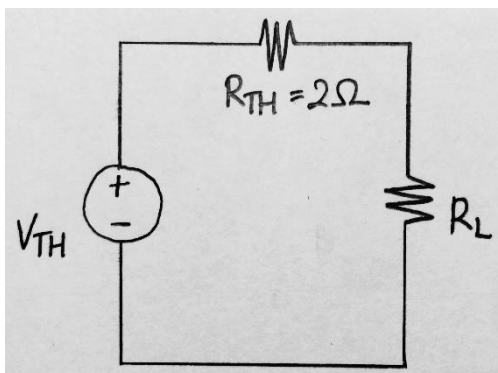

To achieve maximum power transfer to the load,  $R_L = R_{TH} = 2\Omega$ .

The maximum power transfer to the load  $= I^2 R$


$$= (V_{TH}/2R)^2 R$$

$$= V_{TH}^2 / (4R)$$

$$= (-4)^2 / (4 \times 2)$$

$$= 2W$$

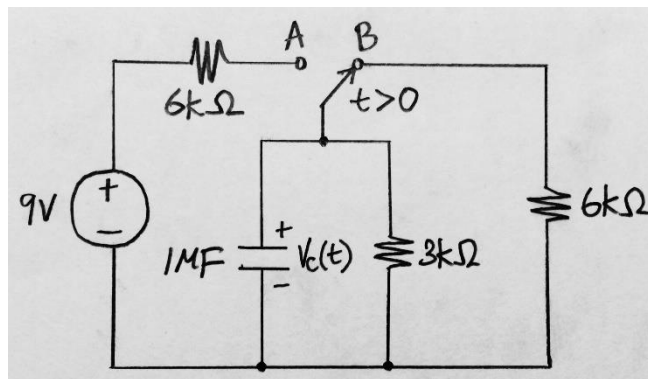2. (a) (i) General solution:  $V_C(t) = K_1 + K_2 e^{-t/\tau}$




To find  $R_{TH}$  across the capacitor for  $t > 0$ , short-circuit the 9V voltage source.

Also, no current flows from the capacitor to A for  $t > 0$  since it is open-circuit.

$$R_{TH} = 3k // 6k$$

$$R_{TH} = 2k\Omega$$
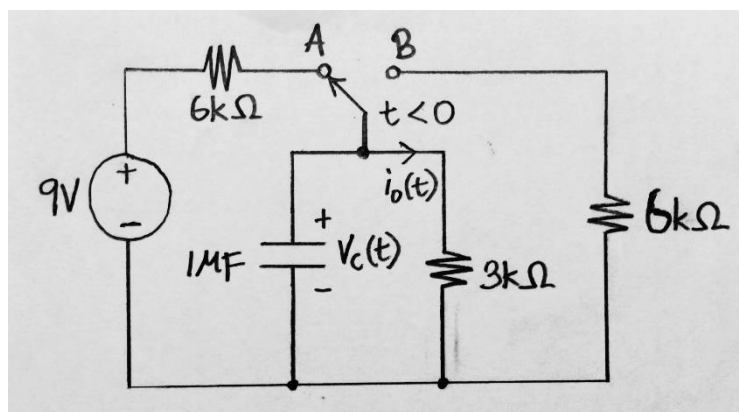
$$\tau = CR_{TH} = (1\mu F)(2k\Omega) = 0.002s$$



At  $t = 0^-$ , capacitor acts like an open-circuit since it is fully charged.

$V_C(0^-) = \text{Voltage across the } 3k\Omega \text{ resistor (parallel)}$

$$V_C(0^-) = \frac{3k}{6k+3k} \times 9V = 3V \quad (\text{potential divider rule})$$

$$V_C(0^+) = V_C(0^-) = 3V \quad (\text{voltage continuity property})$$

Therefore,  $V_C(0) = K_1 + K_2 e^{-(0/\tau)}$

$$3 = K_1 + K_2$$

At  $t = \infty$ , capacitor will be fully discharged.

$$V_C(\infty) = 0$$

$$0 = K_1 + K_2 e^{-(\infty/\tau)}$$

$$0 = K_1 + K_2(0)$$

$$K_1 = 0$$

$$K_2 = 3 - 0 = 3$$



Hence,  $V_C(t) = 3e^{-t/0.002} \text{ V}$ .

$$i_0(t) = \frac{V_C(t)}{3k\Omega}$$

$$i_0(t) = \frac{3e^{-t/0.002}}{3k}$$

$$i_0(t) = e^{-t/0.002} \text{ mA}$$

(a) (ii)

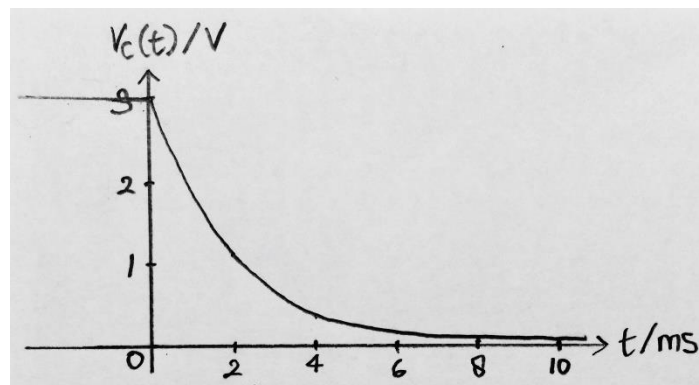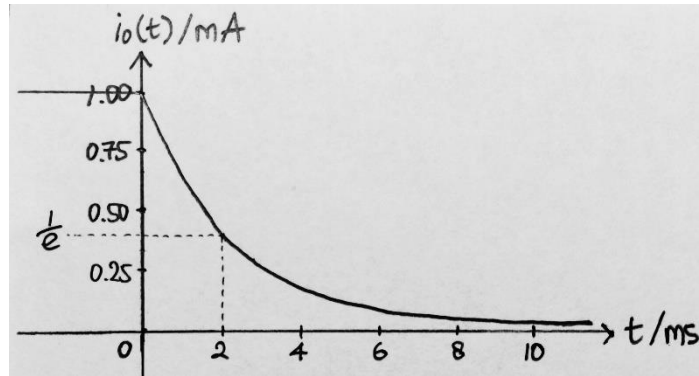

(b) Capacitance across CD

= [(Capacitance across the parallel  $3\mu\text{F}$ ,  $4\mu\text{F}$  and  $3\mu\text{F}$  capacitors) in series with  $10\mu\text{F}$ ]

//  $1\mu\text{F}$  //  $4\mu\text{F}$

$$= 1 / [1 / (3 + 4 + 3) + 1 / 10] + 1 + 4$$

$$= 5 + 1 + 4$$

$$= 10\mu\text{F}$$

$$\tau = R \times C = 1k\Omega \times 10\mu\text{F} = 10\text{ms}$$

3. (a) (i)  $V_2 = -\frac{R_F}{R_1} \times V_{in} = -\frac{20k}{15k} \times 1 = -\frac{4}{3} \text{ V}$

(ii) By potential divider rule,

$$V_- = \frac{5k}{10k+5k} \times V_{out}$$

$$V_- = \frac{1}{3} V_{out}$$

Applying op-amp voltage rule:  $V_+ \approx V_-$

$$V_+ = \frac{1}{3}V_{out}$$

$$V_{out} = 3V_+$$

Use superposition to derive  $V_+$ .

Considering  $V_2$  source alone,  $V_+ = \frac{20k}{10k+20k} \times V_2$

$$V_+ = \frac{2}{3}V_2$$

Considering 4V source alone,  $V_+ = \frac{10k}{10k+20k} \times 4V$

$$V_+ = \frac{4}{3}V$$

Hence,  $V_+ = \frac{2}{3}V_2 + \frac{4}{3}$  (by superposition)

$$V_+ = \frac{2}{3}\left(-\frac{4}{3}\right) + \frac{4}{3}$$

$$V_+ = \frac{4}{9}V$$

$$V_{out} = 3V_+ = 3\left(\frac{4}{9}\right) = \frac{4}{3}V.$$

- (iii) No, there is no voltage distortion in the built circuit because all the values of the output voltage from the two op-amps are within the range of [-15V, 15V].

- (b) (i) The system is memoryless because  $y(t_0)$  depends only on input at  $t = t_0$ .

- (ii) The system is causal because  $y(t_0)$  depends on input only for  $t \leq t_0$ .

- (iii)  $x_1(t) \rightarrow y_1(t) = x_1(t) \sin(2t) \cos(5t/6)$  (1)

$$\text{Let } x_2(t) = x_1(t - t_0)$$

$$x_2(t) \rightarrow y_2(t) = x_2(t) \sin(2t) \cos(5t/6)$$

$$= x_1(t - t_0) \sin(2t) \cos(5t/6)$$

$$\text{From (1), } y_1(t - t_0) = x_1(t - t_0) \sin[(2(t - t_0))] \cos[5(t - t_0)/6]$$

Since  $y_2(t) \neq y_1(t - t_0)$ ,  $y(t)$  is not time-invariant.

- (iv)  $x_1(t) \rightarrow y_1(t) = x_1(t) \sin(2t) \cos(5t/6)$

$$x_2(t) \rightarrow y_2(t) = x_2(t) \sin(2t) \cos(5t/6)$$

$$x_1(t) + x_2(t) \rightarrow [x_1(t) + x_2(t)] \sin(2t) \cos(5t/6)$$

$$= x_1(t) \sin(2t) \cos(5t/6) + x_2(t) \sin(2t) \cos(5t/6)$$

$$= y_1(t) + y_2(t)$$

Hence, the system is additive.

$$x_1(t) \rightarrow y_1(t) = x_1(t) \sin(2t) \cos(5t/6)$$


$$a.x_1(t) \rightarrow a.x_1(t) \sin(2t) \cos(5t/6)$$

$$= a.y_1(t)$$

Hence, the system is also homogeneous.

Therefore, the system is linear since it is additive and homogeneous.

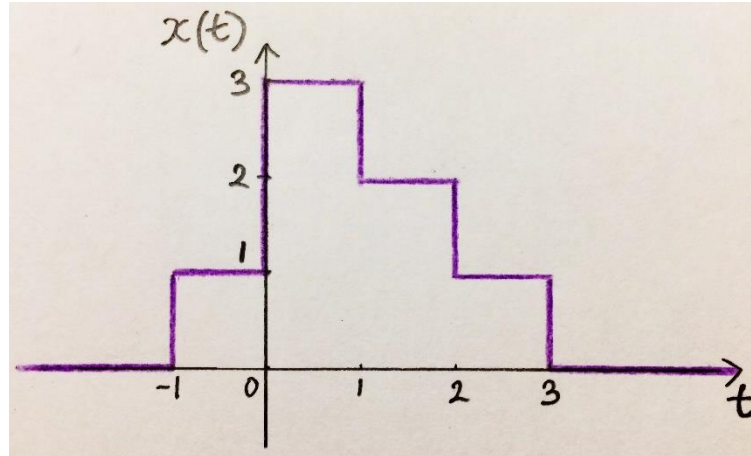4. (a) (i)  $x(t) = u(t+1) + 2u(t) - u(t-1) - u(t-2) - u(t-3)$



(ii)  $x(t)$  is not an even nor an odd function.

$x(t) \neq x(-t)$ , thus  $x(t)$  is not an even function.

$x(t) \neq -x(-t)$ , thus  $x(t)$  is not an odd function.

(b)  $h(t) = u(t-3) - u(t)$ ,  $x(t) = u(t-2)$

Using convolution integral,

$$y(t) = h(t) * x(t) = x(t) * h(t) = \int_{-\infty}^{+\infty} x(\tau)h(t-\tau)d\tau = \int_{-\infty}^{+\infty} h(\tau)x(t-\tau)d\tau$$

$$\begin{aligned} y(t) &= \int_{-\infty}^{+\infty} h(\tau)x(t-\tau)d\tau \\ &= \int_{-\infty}^{+\infty} [u(\tau-3) - u(\tau)][u(t-\tau-2)]d\tau \\ &= \int_{-\infty}^{+\infty} -[u(\tau) - u(\tau-3)][u(t-\tau-2)]d\tau \\ &= -\int_0^3 u(t-2-\tau)d\tau \end{aligned}$$

$$y(t) = \begin{cases} -3, & \text{for } t > 5 \\ -t+2, & \text{for } 2 < t \leq 5 \\ 0, & \text{for } t \leq 2 \end{cases}$$

(c) (i)  $y''(t) + 5y'(t) + 6y(t) - x'(t) - x(t) = 0$

$$y''(t) + 5y'(t) + 6y(t) = x'(t) + x(t)$$

$$\text{Let } x(t) = e^{st}, y(t) = H(s).e^{st}.$$

$$s^2 H(s) e^{st} + 5s H(s) e^{st} + 6H(s) e^{st} = s e^{st} + e^{st}$$

$$H(s) e^{st} (s^2 + 5s + 6) = e^{st} (s + 1)$$

$$H(s) = \frac{s+1}{s^2+5s+6}$$

$$H(s) = \frac{s+1}{(s+2)(s+3)}$$

(ii)  $x(t) = 2.4e^{-t}u(t)$

$$X(s) = \frac{2.4}{s+1} \quad (\text{see Appendix B})$$

$$H(s) = \frac{s+1}{(s+2)(s+3)}$$

$$Y(s) = H(s) \cdot X(s)$$

$$= \frac{s+1}{(s+2)(s+3)} \cdot \frac{2.4}{s+1}$$

$$= 2.4 \left[ \frac{1}{(s+2)(s+3)} \right]$$

$$= 2.4 \left[ \frac{1}{(s+2)} - \frac{1}{(s+3)} \right]$$

$$= \frac{2.4}{(s+2)} - \frac{2.4}{(s+3)}$$

$$y(t) = (2.4e^{-2t} - 2.4e^{-3t})u(t) \quad (\text{see Appendix B})$$