

Solver: CHEN BENJAMIN, WILLIS TEE TEO KIAN, YONG SHAN JIE

1)

a)

i) Required output: $V_{out} = 4V_1 + V_2$

$$V_{out} = \left(1 + \frac{R_f}{R_1}\right) \times V_{in}$$

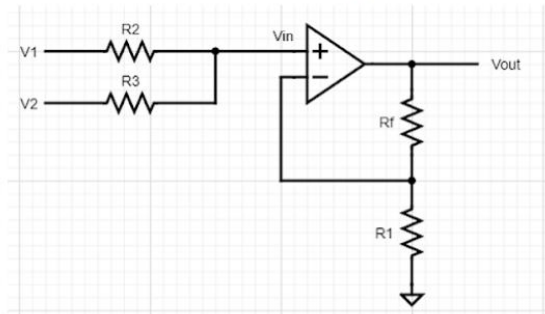


Figure 1. Non-Inverting Amplifier

$$V_{in} = \left(\frac{R_3}{R_2 + R_3}\right) \times V_1 + \left(\frac{R_2}{R_2 + R_3}\right) \times V_2$$

$$V_{in} = \left(\frac{R_3 V_1 + R_2 V_2}{R_2 + R_3}\right)$$

$$V_{in} = \left(\frac{R_3 V_1 + R_2 V_2}{R_2 + R_3}\right)$$

$$\therefore V_{out} = \left(\frac{R_3 V_1 + R_2 V_2}{R_2 + R_3}\right) \left(1 + \frac{R_f}{R_1}\right)$$

$$V_{out} = (R_3 V_1 + R_2 V_2) \left(\frac{1 + \frac{R_f}{R_1}}{R_2 + R_3}\right)$$

In order to obtain $V_{out} = 4V_1 + V_2$:

1) Let $R_3 = 4k\Omega$, $R_2 = 1k\Omega$

2) Let $\left[\frac{\left(1 + \frac{R_f}{R_1}\right)}{R_2 + R_3}\right] = 1 \Rightarrow \left(1 + \frac{R_f}{R_1}\right) = (R_2 + R_3) \Rightarrow \left(1 + \frac{R_f}{R_1}\right) = 5k\Omega$

$R_f = 4k\Omega$, $R_1 = 1k\Omega$

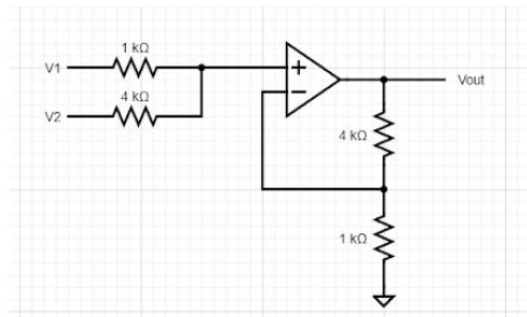


Figure 2. Non-Inverting Amplifier with Resistance value filled

ii) It was clarified during the exam that part i. & ii. can be done together, hence part ii.'s requirement is fulfilled in part i.

- b) Cut-off Frequency of Low Pass Filter $f_{CL} = 80\text{Hz}$

Cut-off Frequency of High Pass Filter $f_{CH} = 0.5\text{Hz}$

Since Magnitude Response shows a Band-pass response with a gain of 20dB at pass-band, an Active Low Pass Filter & Active High Pass Filter is connected in series.

$$20\log_{10}A_{FT} = 20\text{dB}$$

$$\log_{10}A_{FT} = 1\text{dB}$$

$$A_{FT} = 10^1 = 10$$

Total Gain achieved from Active Low Pass & High Pass Filter in series = 10.

Gain of Active Low Pass & High Pass Filter would be $A_{FL} = A_{FH} = \sqrt{10} = 3.162$

$$\text{Using Non Inverting Amplifier, } 3.162 = 1 + \frac{R_{F1}}{R_1} = 1 + \frac{R_{F2}}{R_2}$$

Let $R_1=R_2 = 1\text{k}\Omega$, $R_{F1}=R_{F2} = 2.162\text{k}\Omega$

Given $0.1\mu\text{F}$ capacitors, cut-off frequency is found using the following formula:

$$f_C = \frac{1}{2\pi RC}$$

$$f_{CH} = 0.5\text{Hz} = \frac{1}{2\pi R_H(0.1\mu\text{F})}$$

$$R_H = 3.183\text{M}\Omega$$

$$f_{CL} = 80\text{Hz} = \frac{1}{2\pi R_L(0.1\mu\text{F})}$$

$$R_L = 19.894\text{k}\Omega$$

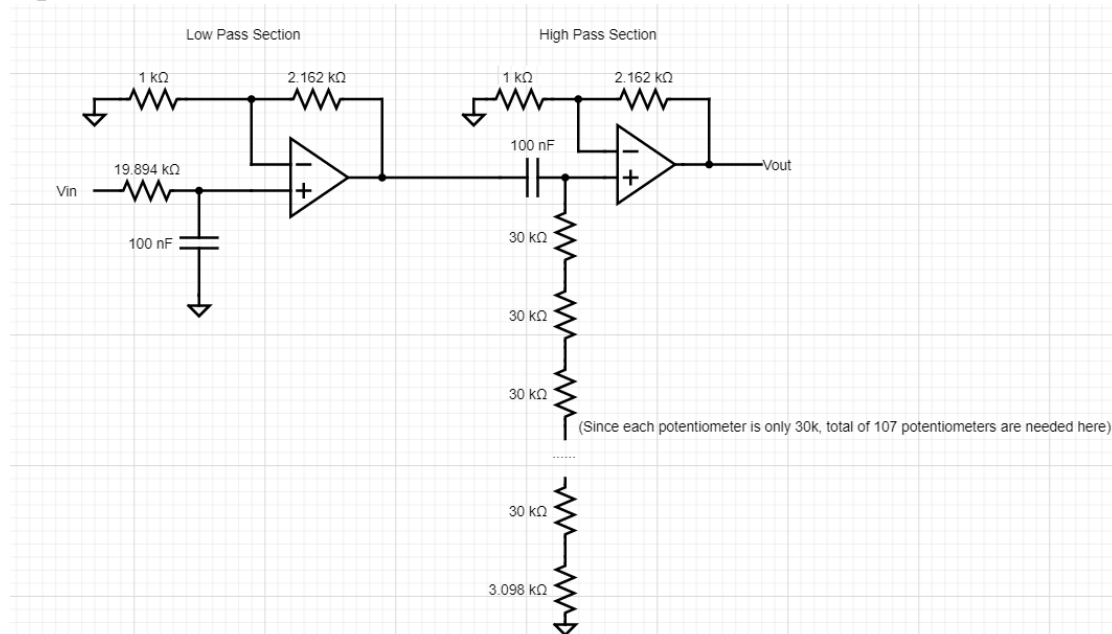


Figure 3. Active Band Pass Filter with a pass band of 0.5Hz - 80Hz, and a total gain of 20dB.

- c) Ultrasound Pulse Generator sends RF Electrical pulses to transducer, thereby activating the transducer. The transducer then generates ultrasound RF pulses (inverse piezoelectric effect), and all reflected ultrasound waves vibrate the same transducer which converts the vibrations into electrical pulses (piezoelectric effect), thereby forming the ultrasonic medical image.

2)

a)

- i) Any term with subscript of 'd' refers to signal (differential mode input), and any term with a subscript of 'c' refers to noise (common mode input).

$$CMRR(dB) = 70dB$$

$$CMRR = 20\log_{10} \frac{A_d}{A_c} = 70$$

$$\log_{10} \frac{A_d}{A_c} = 3.5$$

$$\frac{A_d}{A_c} = 10^{3.5}$$

Using Output SNR Formula: $\frac{V_{od}}{V_{oc}} = CMRR \times \frac{V_{id}}{V_{ic}}$

$$\frac{V_{od}}{1mV} = 10^{3.5} \times \frac{0.005V}{200mV}$$

$$\frac{V_{od}}{1mV} = 79.057$$

$$V_{od} = 0.079V$$

$$\text{Maximum Amplification} = \frac{0.079}{0.005} = 15.81$$

- ii) Slew Rate Formula to ensure that there is no distortion: $2\pi fK \leq SR$, where

$$K = V_{od} = V_{id} \times A_d$$

$$\text{Given } SR = 0.4V/\mu s = 400\,000V/s$$

$$\text{Input Signal } V_{ba} = 0.005\sin(400 \times 10^6 \pi t)$$

$$a\sin 2\pi ft = 0.005\sin(400 \times 10^6 \pi t)$$

$$2\pi fK = (400 \times 10^6) \times 0.079$$

$$2\pi fK = 31\,600\,000\,V/s$$

Since $2\pi fK \geq SR$, output will be distorted.

- iii) Given in question that $R_1 = R_4, R_3 = R_2$ we can exploit the special case of Difference

$$\text{Amplifier: } V_{out} = \left(\frac{R_b}{R_a}\right) \times V_{ba}$$

$$\text{Let } R_b = R_1 = R_4, R_a = R_3 = R_2$$

$$\frac{R_b}{R_a} = 15.81 \rightarrow \text{Letting } R_a = R_3 = R_2 = 1k\Omega, R_b = R_1 = R_4 = 15.81k\Omega$$

b)

$$\text{Dynamic Range (14 bit)} = \text{Desired SNR}(dB) = 20\log_{10} 2^{14} = 84.288dB$$

$$\text{Dynamic Range (12 bit)} = \text{Desired SNR}(dB) = 20\log_{10} 2^{12} = 72.247dB$$

$$\text{Current SNR}(dB) = 20\log_{10} \frac{200mV}{5mV} = 32.04dB$$

$$\text{Additional SNR Required (14 bit)} (dB) = 84.288 - 32.04 = 52.248dB$$

$$\text{Additional SNR Required (12 bit)} (dB) = 72.247 - 32.04 = 40.207dB$$

$$\text{Select between } 3kHz \sim 15kHz, f_c = 3.2kHz$$

$$\text{Number of decades between } 3.3kHz \text{ to } 15kHz \log_{10} \frac{15kHz}{3.2kHz} = 0.671 \text{ Decade}$$

$$\text{Order of Filter (14 Bit): } \text{Ceiling}\left(\frac{52.248dB}{20 \times 0.671dB}\right) = 4th \text{ Order Filter}$$

$$\text{Order of Filter (12 Bit): } \text{Ceiling}\left(\frac{40.207dB}{20 \times 0.671dB}\right) = 3rd \text{ Order Filter}$$

\therefore Minimum order of anti-aliasing filter changes from 4 to 3.

(Note: Answer may vary depending on the value of f_c chosen, but the method is the same)

3)

a)

- i) **True.** The stated expression is a unit-step function. Performing a z-transform followed by applying geometric series formula on the expression will give you $11-z^{-1}$ or zz^{-1}
- ii) **False.** One-sided z-transform starts from $k=0$, not $k=-\infty$
- iii) **False.** When examining the poles, it is said to be stable if all the poles fall within the unit circle.
- iv) **False.** A system is critically stable if there is only 1 pole on the unit circle. Multiple poles on the unit circle indicates that the system is unstable.
- v) **False.** The concept to determine the stability of a closed-loop system is Jury Stability Test. Ziegler Nichols method is heuristic PID tuning method.

b) i)

$$y(k-2) - 0.4y(k-1) + 0.03y(k) = u(k-2)$$

Assuming Sampling Interval $T=1$, applying Shifting Theorem to the respective terms:

$$y(k-2) \Rightarrow z^{-2}Y(z)$$

$$0.4y(k-1) \Rightarrow 0.4z^{-1}Y(z)$$

$$0.03y(k) \Rightarrow 0.03Y(z)$$

$$u(k-2) \Rightarrow z^{-2}U(z)$$

$$\text{Hence, } Z[y(k-2) - 0.4y(k-1) + 0.03y(k)] = Z[u(k-2)]$$

$$z^{-2}Y(z) - 0.4z^{-1}Y(z) + 0.03Y(z) = z^{-2}U(z)$$

$$Y(z)(z^{-2} - 0.4z^{-1} + 0.03) = z^{-2}U(z)$$

Transfer function is expressed in terms of output over input, $\frac{Y(z)}{U(z)}$.

$$\frac{Y(z)}{U(z)} = \frac{z^{-2}}{z^{-2} - 0.4z^{-1} + 0.03}$$

Multiplying Numerator & Denominator by z^2 ,

$$\frac{Y(z)}{U(z)} = \frac{1}{1 - 0.4z + 0.03z^2}$$

ii)

$$Y(z) = \frac{1}{1 - 0.4z + 0.03z^2} U(z)$$

Given that $u(k)$ is a unit step function, $U(z) = \frac{z}{z-1} = \frac{1}{1-z^{-1}}$

$$Y(z) = \frac{1}{1 - 0.4z + 0.03z^2} \left(\frac{1}{1-z^{-1}} \right)$$

Using Initial Value Theorem: $y(0) = \lim_{z \rightarrow \infty} Y(z)$

$$y(0) = \frac{1}{1 - 0.4\infty + 0.03(\infty)^2} \left(\frac{1}{1-\frac{1}{\infty}} \right)$$

$$y(0) = \frac{1}{1 - 0.4\infty + 0.03(\infty)^2} \left(\frac{1}{1-0} \right)$$

$$y(0) = \frac{1}{\infty} = 0$$

Initial value = 0

$$\text{iii) Transfer function: } \frac{Y(z)}{U(z)} = \frac{1}{1 - 0.4z + 0.03z^2}$$

Solving for the poles by finding the roots after letting denominator

$$0.03z^2 - 0.4z + 1 = 0$$

$$z = 10 \text{ or } z = 3.33$$

Since both poles ≥ 1 , the system is unstable.

4)

a)

Let Transfer Function of System = $G(z)$

Transfer function of Digital Control System $\frac{Y}{Y^*} = \frac{KG(z)}{1+KG(z)}$

$$\frac{Y}{Y^*} = \frac{K \left[\frac{1}{(z-0.1)(z-0.2)} \right]}{1+K \left[\frac{1}{(z-0.1)(z-0.2)} \right]}$$

$$\frac{Y}{Y^*} = \frac{K}{(z-0.1)(z-0.2)+K}$$

$$\frac{Y}{Y^*} = \frac{K}{z^2-0.3z+0.02+K}$$

Characteristic equation: $z^2 - 0.3z + 0.02 + K$

Comparing it with the standard characteristic equation:

$$z^2 - 2\cos(\omega_n T) \sqrt{1-\zeta^2} e^{-\zeta\omega_n T} z + e^{-2\zeta\omega_n T}$$

We can see that:

$$e^{-2\zeta\omega_n T} = 0.02 + K$$

To achieve $\zeta = 0.5$, $\omega_n = 4$ given $T = 0.1$,

$$e^{-2(0.5)(4)(0.1)} = 0.02 + K$$

$$K = 0.6703 - 0.02$$

$$K = 0.6503$$

b)

Characteristic equation: $z^2 - 0.3z + 0.02 + K$

Since Characteristic Equation is a 2nd Order Polynomial, highest term is a_2

$$a_0 = 1, a_1 = -0.3, a_2 = 0.02 + K$$

Criterion 1: $|a_n| < a_0$

$$|a_2| < a_0$$

$$|0.02 + K| < 1$$

$$-1.02 < K < 0.98$$

Criterion 2: $P(1) > 0$

$$(1)^2 - 0.3(1) + 0.02 + K > 0$$

$$(1)^2 - 0.3(1) + 0.02 + K > 0$$

$$K > -0.72$$

Criterion 3: $P(-1) > 0$ if n is even, $P(-1) < 0$ if n is odd

Since $n = 2$, $P(-1) > 0$

$$(-1)^2 - 0.3(-1) + 0.02 + K > 0$$

$$K > -1.32$$

Combining the inequalities, $-0.72 < K < 0.98$

--End of Answers--