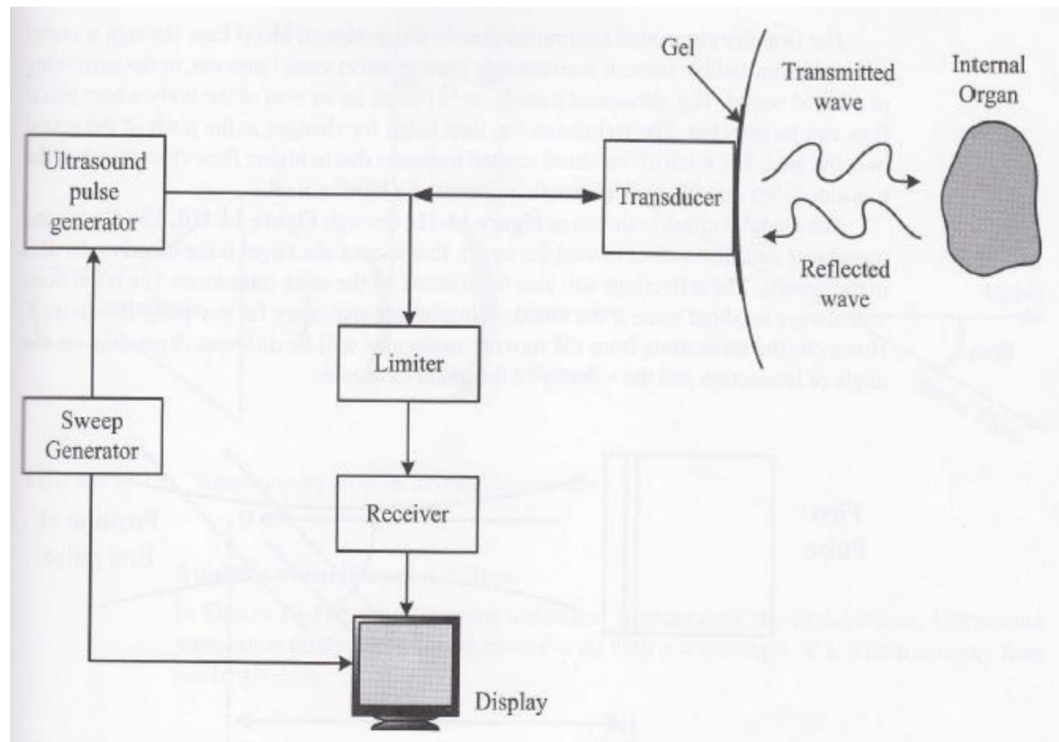


Solver: Boppana Kavya Sri

Email Address: KAVYASRI001@e.ntu.edu.sg

1. (a)



Block diagram of Ultrasound System

(b)

Firstly we have to find the range of V_{ab} to design suitable signal conditioning circuit to get desired V_{out} .

As the range of V_{ab} depends on the value of RTD at different temperatures, we have to find the value of RTD at 125°C and 250°C.

$$RTD \text{ at } 125^{\circ}\text{C} = 100 [1 + 0.005 (125 - 100)] = 112.5$$

$$RTD \text{ at } 250^{\circ}\text{C} = 100 [1 + 0.005 (250 - 100)] = 175$$

We find that the given circuit is Wheatstone bridge, hence

$$V_{ab} = (RTD \times 150 - 150 \times 150) / ((150 + RTD) (150 + 150))$$

$$V_{ab} \text{ at } 125^{\circ}\text{C} = -0.07$$

$$V_{ab} \text{ at } 250^{\circ}\text{C} = 0.038$$

From the question we understand that -0.07 and 0.038 has to be amplified and shifted to get V_{out} as 0.1 and 10

Let us assume that the equation is in form of
 $y=mx+c$ where y is output voltage, x is input voltage of signal conditioning circuit.

$$0.1=m(-0.07)+c$$


$$10=m(0.038)+c$$

Solving the equations, we get signal conditioning equation as:

$$y=(-91.65)x+(-6.52) \Rightarrow y=-(91.67(x)+6.52) \text{ ----- eq.(1)}$$

Summation amplifier can be used to obtain the desired signal conditioning circuit as below:
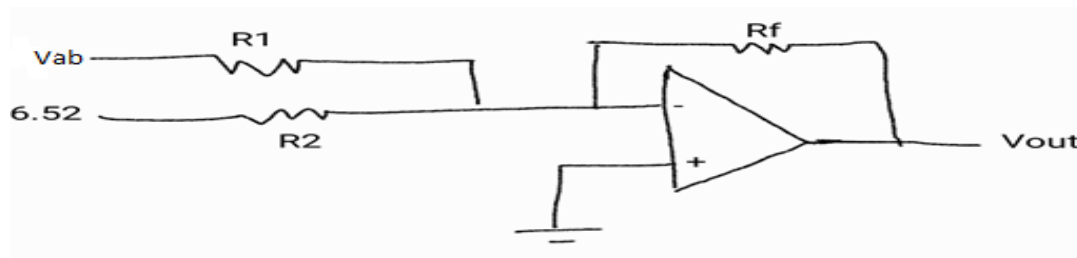
$$V_{out} = -(R_f/R_1 (V_{ab}) + R_f/R_2 (6.52)) \text{ -----eq.(2)}$$



Hence the resistors can be chosen such that $R_f/R_1=91.67$ and $R_f/R_2=1$ by comparing eq.(1) and eq.(2), therefore we can get many combinations of them. For e.g.: choose $R_f = R_2 = 100\Omega$ then $R_1= 1.09\Omega$.

2.

- a) Slew Rate = $0.6V/\mu s$
 $V_{in} = 0.2 \sin(10^3 t)$ volt

$$V_{out} = |(120k/R_1)| V_{in}$$

$$= (120k/R_1) (0.2 \sin(10^3 t))$$

$$\text{Here } K = (120k/R_1)0.2$$

$$\omega = 10^3$$

The minimum value of R_1 required for the op-amp to avoid distortion due to slew rate limitation can be found using the condition:

$$\omega \leq SR/K$$

$$10^3 \leq (0.6 \times R_1)/(10^{-6} \times 120k \times 0.2)$$

$$R_1 \geq 40$$

Hence minimum value of R_1 is 40Ω .

- b) Another equation that has to be satisfied for the output to be not distorted is :

$$-15V \leq V_{out} \leq 15V$$

Max value of $V_{out} = (120k/R_1)0.2$

Putting min value of R_1 we get

$V_{out} = (120k/40)0.2 = 600V$ which is not less than 15V, hence output distortion will occur for the minimum value of R_1 computed in part (a).

To avoid output distortion we should have

$$(120k/R_1)0.2 \leq 15$$

Hence minimum value of R_1 that will avoid distortion is 1.6k Ω .

- c) The first half of the given circuit acts like low pass filter

$$f_H = 1/(2 \pi R C)$$

$$= 1/(2 \times 3.14 \times 1.2k \times 0.01\mu)$$

$$= 10^3/(2 \times 3.14 \times 1.2 \times 0.01)$$

$$= 13.269k \text{ Hz}$$

All the frequencies less than 13.269k Hz will be passed by this first half of the circuit.

The second half of the given circuit acts like high pass filter

$$f_L = 1/(2 \pi R C)$$

$$= 1/(2 \times 3.14 \times 1k \times 0.1\mu)$$

$$= 10^3/(2 \times 3.14 \times 0.1)$$

$$= 1.592k \text{ Hz}$$

All the frequencies greater than 1.592k Hz will be passed by this second half of the circuit.

Hence the circuit shown in the question acts like Band Pass Filter with pass band

$$1.592k \leq f \leq 13.269k.$$

- d) • Signal bandwidth = 0 to 3k Hz
• Noise from 20kHz \Rightarrow Stopband should begin at 20kHz

$$\bullet \text{ So } (f_{SIG} = 3kHz) < f_C < (f_1 = 20kHz)$$

- select f_C to be 3.2kHz (to begin with)

Signal: 200mV; Noise = 10 mV(from 20kHz)

$$\text{SNR of input signal} = 20 \log 200/10 = 26\text{dB}$$

$$\text{Additional SNR needed} = 80 \text{ dB} - 26 \text{ dB} = 54 \text{ dB (i.e.)}$$

Noise needs to be attenuated by 54 dB)

$$3.2kHz \text{ to } 20kHz = \log_{10}(20k/3.2k) = 0.795 \text{ Decade}$$

$$N = (54\text{dB}/0.795)/(20\text{dB}) = 3.39 \Rightarrow 4\text{th order}$$

Minimum order of filter needed is four.

3. a)

i)

Assume that y is z-transformable and the z-transform of $y(k)$ is $Y(z)$ and set the sampling interval to 1.

$u(k)$ is a unit step function that shifted to the right by 1. The Z-transform of unit step function is $z/(z-1)$, so $Z[u(k)] = 1/(1-z)$

Let us find out $y(1)$ using the difference equation and we know that $u(k) < 0 = 0$ as it is z-transformable and $u(0)=1$, $u(1)=0.5142$, $u(2)=-0.5142$, and $u(k)=0$, $k=3,4,5,\dots$

Let us substitute -1 in place of k in difference equation, then we get:

$$y(1) - 1.5241y(0) + 0.5241y(-1) = 0.5241u(0) + 0.2642u(-1)$$

$$\text{Hence } y(1) = 0.5241$$

Apply shifting theorem to find the z-transform of difference equation

$$Z[y(k+2)] = z^2 * [Y(z) - y(0) - z^{-1}y(1)] = z^2 * Y(z) - z(0.5241)$$

$$Z[y(k+1)] = z * [Y(z) - y(0)] = z * Y(z)$$

$$Z[u(k+1)] = z * [U(z) - u(0)] = (z/1-z) - z$$

So the difference equation can be written as:

$$z^2 * Y(z) - z(0.5241) - 1.5241z Y(z) + 0.5241 Y(z) = 0.5241((z/1-z) - z) + 0.2642(1/1-z)$$

$$Y(z) = (0.5241z + 0.2642) / (-z^3 + z^2 + z - 1) \text{ is the Z transform.}$$

ii)

$$\text{We know } y(0)=0, y(1)=0.5241$$

when k=0 the difference equation becomes

$$y(2) - 1.5241y(1) = 0.5241 * 0.5142 + 0.2642$$

$$y(2) = 1.33$$

b)

$$\text{Given } K_u=10 \text{ and } P_u=0.1 \text{ sec}$$


$$P=0.6K_u=6$$

$$I=0.5P_u=0.05$$

$$D=0.125P_u=0.0125$$

Ziegler-Nichols Tuning Method

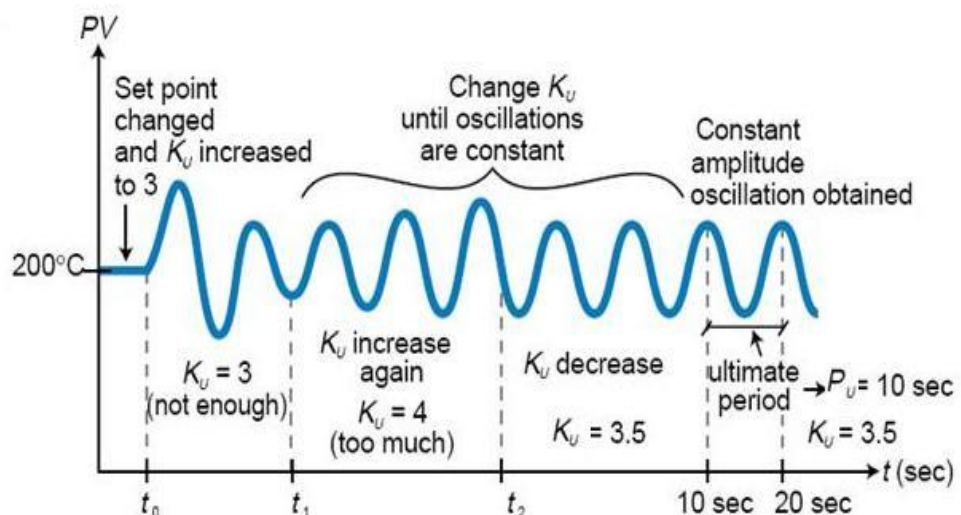- Switch off the integral and derivative control .
- Increase the proportional gain until the response oscillates with constant amplitude, then the period is ultimate period and gain is ultimate gain at that point.



4.

a) Open loop stability:

The poles of the equation lies in the equation:

$$G(z)=(z-0.5141)(z-1) \Rightarrow z=0.5141 \text{ or } 1.$$

We find that one pole is less than one and another is equal to 1. Hence single pole lies on unit circle which makes the system critically stable.

b) $P(z) = 1 + K G(z)$
 $= 1 + K(0.5142z + 0.2642) / ((z - 0.5142)(z - 1))$

$P(z)=0$ is the characteristic equ then:

$$z^2 + (0.5142K - 1.5142)z + 0.2642K + 0.5142 = 0$$

According to Jury Stability Test when a system is stable following conditions apply:

$$A_0=1, A_1=(0.5142K-1.5142), A_2=0.2642K+0.5142$$

- i. $A_0 < 0$ True
- ii. $|A_2| < A_0$ $|0.2642K + 0.5142| < 1$
 $-5.73 < K < 1.839$
- iii. At $z=1$ the equation > 0
 $1 + 0.5142K - 1.5142 + 0.2642K + 0.5142 > 0 \Rightarrow K > 0$
- iv. At $z=-1$ the equation > 0 (even)
 $1 - 0.5142K + 1.5142 + 0.2642K + 0.5142 > 0 \Rightarrow K < 12.11$

$$0 < K < 1.839$$

Either iii. or iv. equation should be 0 for the system to be critically stable. Hence for $K=0$, 1.839 it is possible.

c) $T = 0.01s$

The characteristic equation when $K=1$ will become :

$$z^2 + (0.5142 - 1.5142)z + 0.2642 + 0.5142 = 0$$

$$z^2 - z + 0.2642 + 0.5142 = 0$$

$$z^2 - z + 5.4062 = 0$$

$$2 \cos(\omega_n T \sqrt{1 - \zeta^2}) e^{-\zeta \omega_n T} = 1$$

$$e^{-2\zeta \omega_n T} = 5.4062$$

$$\zeta \omega_n = \frac{\ln 5.4062}{2 * 0.01}$$

$$\text{Settling time} = T_s = \frac{4}{\zeta \omega_n} = 0.0474s$$

For reporting of errors and errata, please visit pypdiscuss.appspot.com

Thank you and all the best for your exams! ☺
