

Question 1

1)

a) $0x810 = 1000\ 0001\ 0000\ 1100$

i) Unsigned = 33036

ii) Sign-magnitude = -268

iii) Two's complement = -32500

b) $128 < 150 < 255 = 8$ bits for integer part

$0.0625 < 0.1 < 0.125 = 4$ bits for fraction part

Minimum number of bits store each value = 12 bits

$$\begin{aligned}
 c) \quad F &= [(u + v w') (u' x + w)' + x (u' v')']' \\
 &= [(u + v w') (u' x + w)']' [x (u' v')']' \\
 &= [(u + v w')' + (u' x + w)] [x' + (u' v')] \\
 &= [u' + (v w')' + u' x + w] [x' + u' v'] \\
 &= [u' + (v' + w) + u' x + w] [x' + u' v'] \\
 &= [u' v' + u' w + u' x + w] [x' + u' v'] \\
 &= [u' v' x' + u' w x' + 0 + w x'] + [u' v' + u' w v' + u' x v' + w u' v'] \\
 &= u' v' (x' + 1 + w + x + w) + (u' + 1) w x' \\
 &= u' v' + w x'
 \end{aligned}$$

d)

i) $0x49 = 0100\ 1001$

$0xB6 = 1011\ 0110$

$$\begin{array}{r}
 0100\ 1001 \\
 + \quad 1011\ 0110 \\
 \hline
 1111\ 1111 \quad - \text{no overflow}
 \end{array}$$

$0xF3 = 1111\ 0011$

$0x7A = 0111\ 0110$

2's complement of $0x7A = 1000\ 0110$

$$\begin{array}{r}
 1111\ 0011 \\
 + \quad 1000\ 0110 \\
 \hline
 10111\ 1001 \quad - \text{overflow}
 \end{array}$$

- ii) Arithmetic overflow occurs when an arithmetic operation between two N-bit operands produces a result that cannot be sufficiently represented by N bits.
- Rule to detect overflow in 2's complement addition:
- No overflow occurs if the two operands have opposite signs.
 - Overflow is detected when operands have the same signs, but the sum has an opposite sign.


For subtraction, no overflow occurs if the operands have the same signs.

Question 2

2)

a)

i)

 

- ii) The purpose of input E^* is to enable or disable the circuit. When the E^* is asserted, i.e. E^* is active low, the circuit is enabled, and the outputs are allowed to change in response to changes in the inputs. When the E^* is negated, i.e. E^* is active high, the circuit is disabled and the outputs are not allowed to change.

b)

c,d

	00	01	11	10
00	1	1	0	1
01	1	0	X	0
11	1	1	1	0
10	X	1	0	X

$$F(a,b,c,d) = (a + b' + d') (a + c' + d') (b' + c' + d) (a' + b + c')$$

- c)
- Tristate. Two or more outputs can be connected together. However, at any time only one (or no) output should be enabled. Otherwise, it can lead to bus contention and damage the devices.
 - When the inputs of all four logic gates are logical high, namely OR gate, NOT gate, NAND gate and XOR gate, the output is logical high. When any inputs of these four logic gates are logical low, the output is logical low.
 - $X = (A + B) (C D)' E' (F G' + F' G)$
- d)
- t_r – rise time from 10% of V_{DD} to 90% of V_{DD}
 - t_f – fall time from 90% of V_{DD} to 10% of V_{DD}
 - t_{PHL} – propagation delay when output changes from high to low
 - t_{PLH} – propagation delay when output changes from low to high

Question 3

- 3)
- False – Modules can contain code to describe hardware and instances of other modules
False – Regs can only be assigned to from within always blocks
True – For the statements in an always block, the order matters
True – A n input multiplexer requires a $\log_2(n)$ – bit select
True – A parameter is a constant that is local to a module

- b)
- 

- ```
assign F = ((~x&~y&z) | (x&y&~z)) ? 1 : 0;
```

```

c) module ALU (input [30:0] a, b,
 input [2:0] OP,
 output reg [31:0] ALU_OUT);

 always @ *

 case (OP)

 3'b000 : ALU_OUT = A + B;

 3'b001 : ALU_OUT = A - B;

 3'b010 : ALU_OUT = A & B;

 3'b011 : ALU_OUT = A | B;

 3'b100 : ALU_OUT = A ^ B;

 default : ALU_OUT = 32'b0;

 endcase

 endmodule

```

#### Question 4

4)


- a) Level-sensitive D-latch -if enable is high, the input is passed through to the output, which is called transparent and if enable is low, the output is held

| E(Enable) | D (input) | Q (output) | Function    |
|-----------|-----------|------------|-------------|
| 0         | X         | Q          | Store       |
| 1         | 0         | 0          | Transparent |
| 1         | 1         | 1          | Transparent |

Edge-triggered D-flip-flop – at each clock rising edge each flip flop will take its D input and produce that value on its Q output.

| Clk (Clock) | D (Input) | Q (Output) | Function   |
|-------------|-----------|------------|------------|
| 0           | X         | Q          | Store      |
| 0 -> 1      | 0         | 0          | Take value |
| 0 -> 1      | 1         | 1          | Take value |
| 1           | X         | Q          | Store      |


timing diagram

 

b)

i)

Input:  $Z_n$   
Output: Count

 

ii) The output Count = 000

```

iii) module counter (input CLK, RESET,
 input In, output [2:0] Count);
 reg [2:0] nst = st;
 assign Count = st;
 always @ (posedge clk)
 begin
 if (RESET)
 st <= 3'b000;
 else
 st <= nst;
 end

 always @ *
 begin
 nst = st;
 case (st)
 3'b000:
 begin
 if (In)
 nst = 3'b001;
 else
 nst = 3'b010;
 end
 3'b001:
 begin
 if (In)
 nst = 3'b011;
 else
 nst = 3'b010;
 end
 3'b010:
 begin
 if (In)
 nst = 3'b011;
 else
 nst = 3'b100;
 end
 3'b011:
 begin
 if (In)
 nst = 3'b101;
 else
 nst = 3'b100;
 end
 end
 end
end

```

```

 3'b100:
 begin
 if (In)
 nst = 3'b101;

 else
 nst = 3'b110;
 end
 3'b101:
 begin
 if (In)
 nst = 3'b111;

 else
 nst = 3'b110;
 end
 3'b110:
 begin
 if (In)
 nst = 3'111;

 else
 nst = 3'b110;
 end
 3'b010:
 nst = 3'b011;
 endcase
 end
endmodule

```

==End of Answers==

Solver: Wu Ziang

Email Address ZWU018@e.ntu.edu.sg