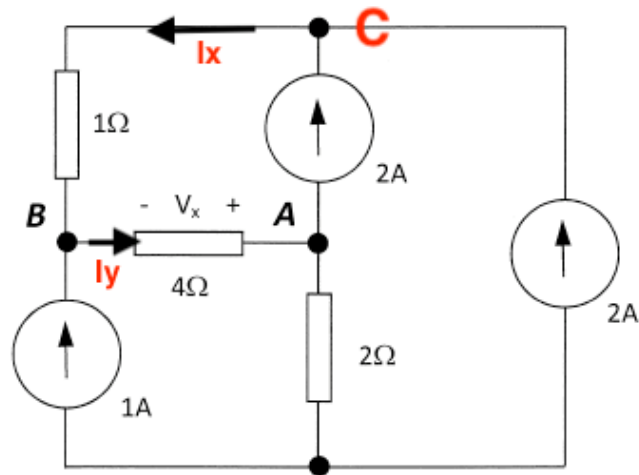


Solver: Fienny Angelina


1)

a)



The fastest way is to use node analysis. On node C,  $I_x = 2 + 2 = 4$ . Furthermore, on node B:  $I_y = I_x + 1 = 5$  A. Thus,  $V_x = -I_y * 4 = 20$  V. (Note that the minus sign is there because the direction of the current is opposed to the direction from A to B. Current flows from higher voltage to lower voltage. Thus, V at B is higher than V at A).

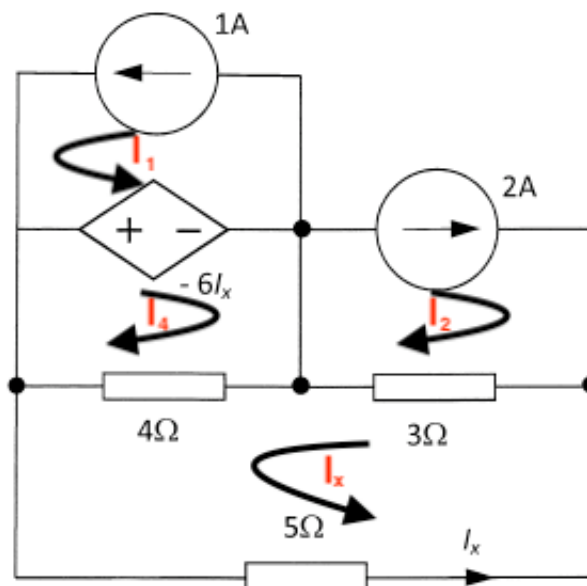- b) Use Mesh Analysis. Number of circuit element = 6, Number of nodes = 3,  
Number of equations =  $6 - 3 + 1 = 4 - 2$  (number of known current) = 2.




At  $I_4$ ,  $4 * I_4 + (-6 * I_x) = 0$ . Thus,  $I_4 = 1.5(I_x)$ .

At  $I_x$ :

$$5 * I_x + 3 (I_x + I_2) + 4 (I_x + I_4) = 0$$

Substituting result from  $I_4$  and the fact that  $I_2 = 2$ , we will obtain  $I_x = -1A$ .

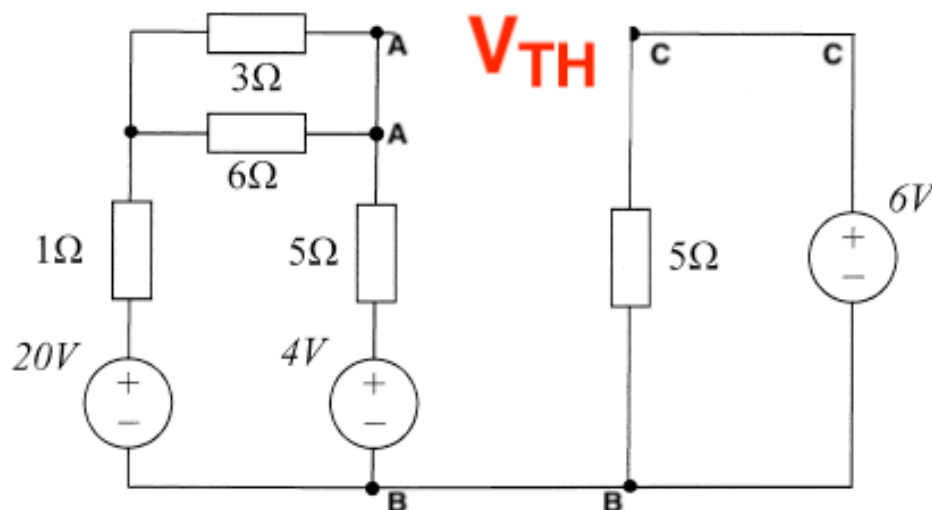- c) Use Thevenin Theorem to calculate  $V_{TH}$  and  $R_{TH}$ .



$$V_{TH} = V_{AB} + V_{BC}$$

We know from the picture that  $V_{BC} = -6V$ .


To calculate  $V_{AB}$ , we need to know  $I_{AB}$ .

$$I_{AB} = \frac{V_{Total}}{R_{Total}} = \frac{20-4}{1+3 \parallel 6+5} = \frac{16}{8} = 2$$

$$V_{AB} = I_{AB} * 5 + 4 = 14V$$

$$V_{TH} = V_{AB} + V_{BC} = 14 + (-6) = 8V.$$

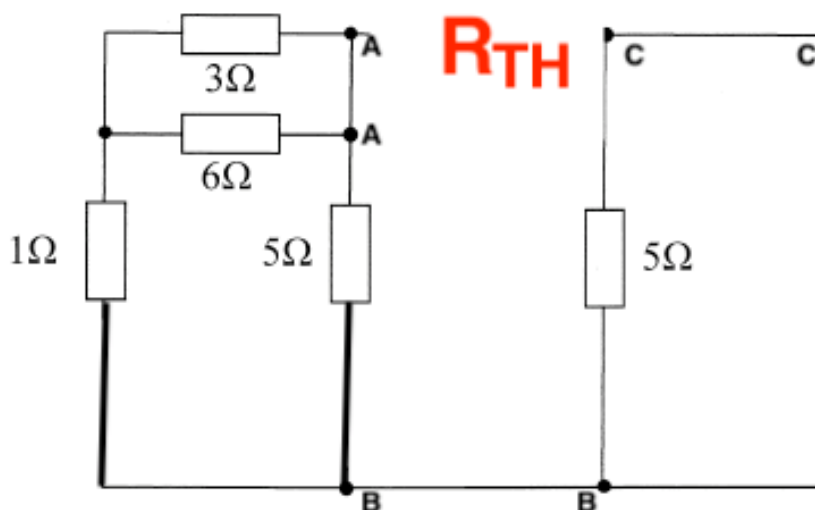To calculate  $R_{TH}$ , we will short circuit all voltage source.



$$R_{TH} = R_{AB} + R_{BC}$$

$$R_{TH} = (3 \parallel 6) + 5 + 1 + 0 = 8$$


For maximum power transfer,

$$R_L = R_{TH} = 8 \text{ ohm}$$


$$P_L = \left( \frac{V_{TH}}{2} \right)^2 \frac{1}{R} = 2 \text{ W}$$

2)

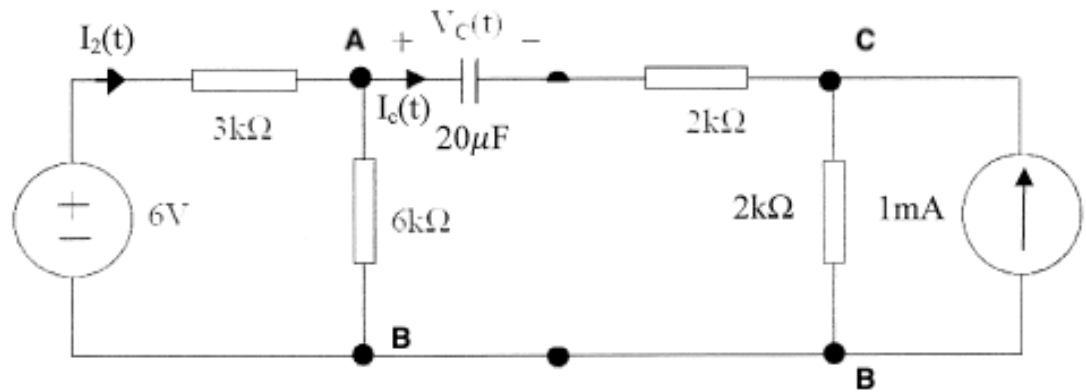a) Below is the drawing of the circuit when  $t < 0$ .



Below is the drawing when  $t \geq 0$ .

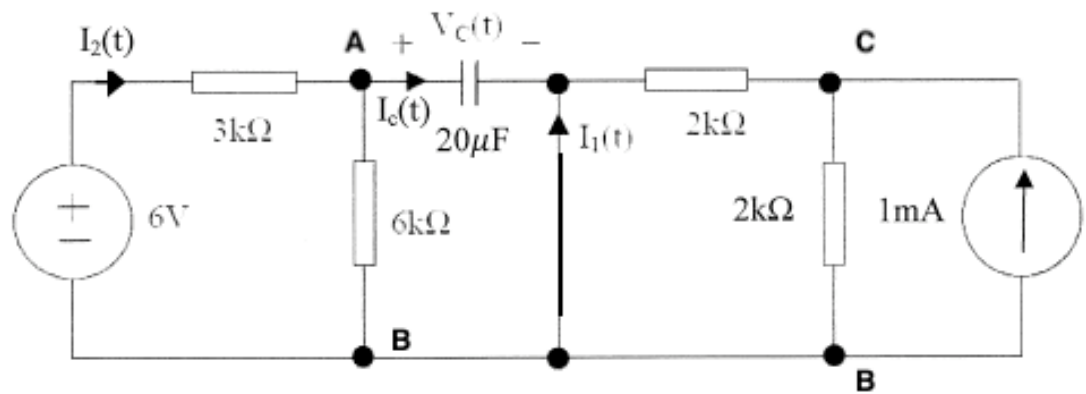


General solution:  $V_c(t) = K_1 + K_2 e^{-t/\tau}$

Find the unknown constants  $K_1$ ,  $K_2$ ,  $\tau$ .

$$\tau = R_{TH}C$$

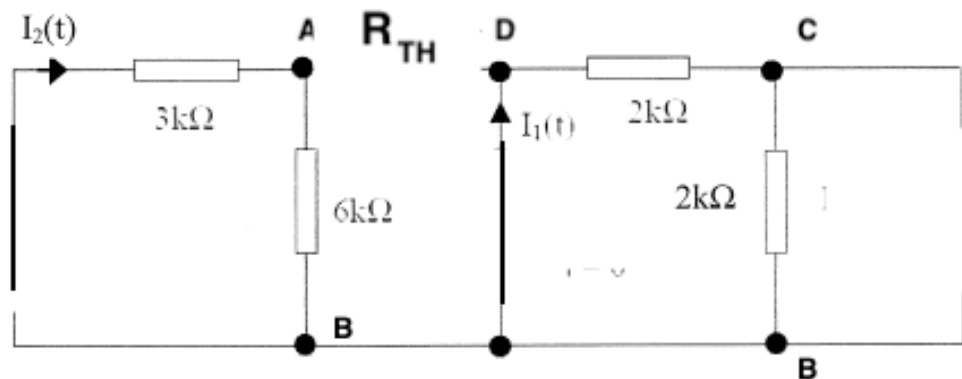Since we only have independent source, we can calculate  $R_{TH}$  directly.




$$R_{TH} = 3 \parallel 6 + 0 = 2 \text{ Kohm}$$

$$\tau = R_{TH}C = 2000 * 20 * 10^{-6} = 0.04$$

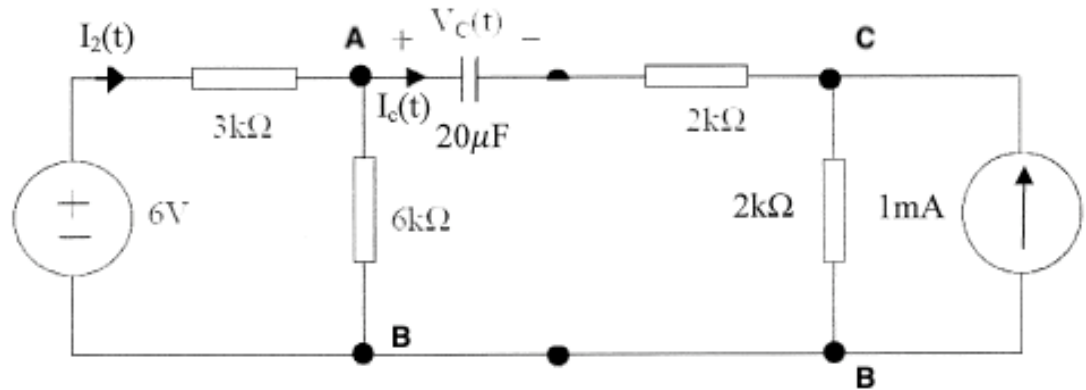**Initial condition,**

$$V_C(0^+) = V_C(0^-)$$

Before  $t = 0$ , capacitor is fully filled, thus no current pass through the capacitor. Below is again the circuit drawing when  $t = 0$ .



$$V_C(0^-) = V_{AB} + V_{BC}$$


$$V_C(0^-) = 6 * \left( \frac{6}{3+6} \right) + 2k\Omega * (-1mA) = 2$$

$$V_C(0^+) = V_C(0^-) = 2$$

Put the result for  $V_C(0^+)$  to the general solution,

$$V_C(0^+) = K_1 + K_2 = 2$$

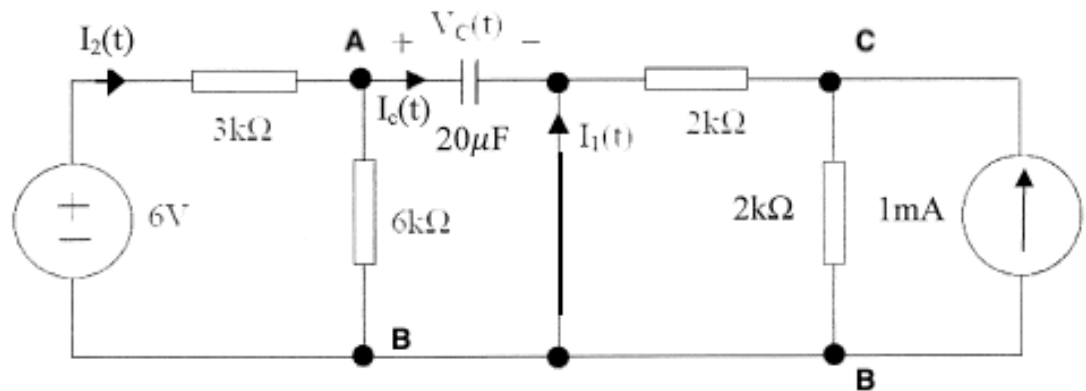Final condition, capacitor is fully filled, thus no current pass through the capacitor.



$$V_C(\infty) = V_{AB} + V_{BC}$$

$$V_{AB} = 6 * \left( \frac{6}{3+6} \right) = 4V$$

$$V_{BC} = -I_{CB} * 2k = -0.5mA * 2k = -1V$$

Note that  $I_{CB} = \frac{I_{Source}}{2}$  through the current division rule. (The current source supports 2 resistors with same resistance in parallel).

$$V_C(\infty) = V_{AB} + V_{BC} = 4 - 1 = 3V$$

Put this back to the general solution:


$$V_C(\infty) = K_1 = 3V$$

Thus, we know that  $K_2 = 2 - K_1 = -1$

i) Substituting every variable to the general solution, we shall obtain:

$$V_C(t) = -1 + 2e^{-t/0.04}$$

ii) When  $t > 0$ ,

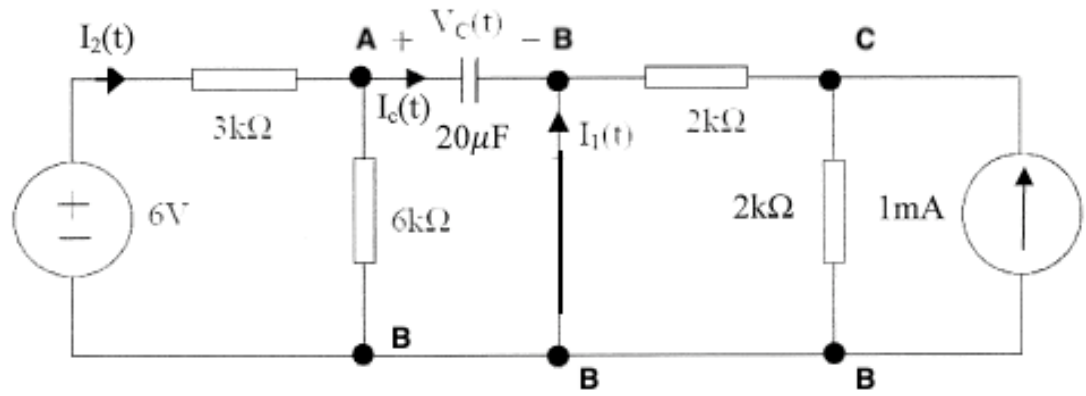

Looking at the loop in the top left corner:

$$6 = I_2 * 3k + V_{AB}$$

We know that:  $V_{AB} = V_C(t)$  when  $t > 0$ .

Thus,


$$6 = I_2 * 3k + V_C(t)$$

$$I_2 = \frac{6 - V_C(t)}{3000} A$$


$$I_2 = \frac{6 - (-1 + 2e^{-\frac{t}{0.04}})}{3000} A$$

$$I_2 = \frac{7 - 2e^{-\frac{t}{0.04}}}{3000} A$$

b) First, let's simplify the circuit.

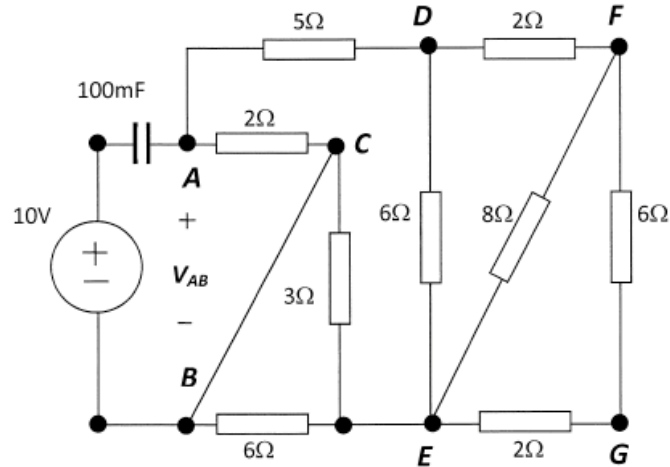

We can redraw the circuit:

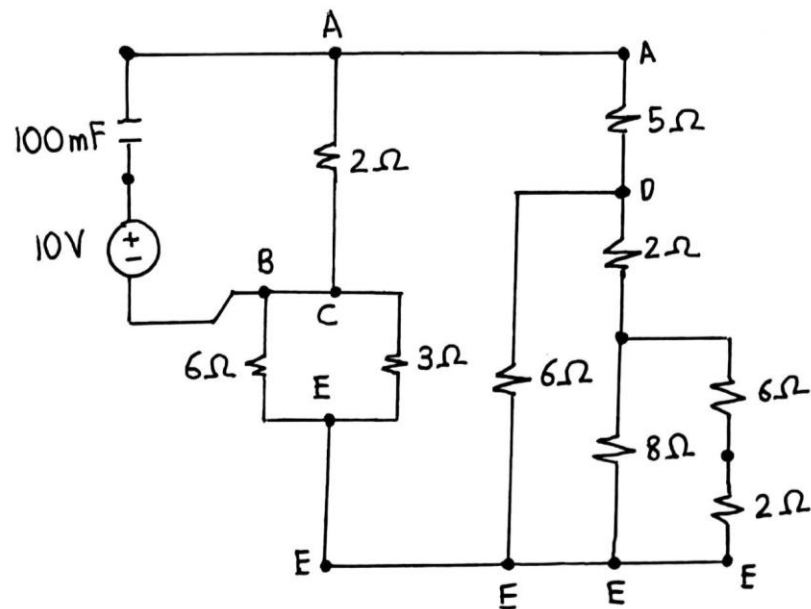

$$R_{FGE} = 6 + 2 = 8 \text{ ohm}$$

$$R_{FE} = R_{FGE} \parallel 8 = 8 \parallel 8 = 4 \text{ ohm}$$

$$R_{DFE} = 2 + R_{FE} = 2 + 4 = 6 \text{ ohm}$$

$$R_{DE} = 6 \parallel R_{DFE} = 3 \text{ ohm}$$

$$R_{ADE} = 5 + R_{DE} = 8 \text{ ohm}$$

$$R_{CE} = 6 \parallel 3 = 2 \text{ ohm}$$

$$R_{AC/AB} = (R_{CE} + R_{ADE}) \parallel 2 = 10 \parallel 2 = \frac{5}{3} \text{ ohm}$$

$$\tau = R_{AB} * C = \frac{5}{3} * 0.1 = \frac{1}{6}$$

Assume that the circuit is connected when  $t = 0$ , then  $V_c(0^+) = 0$ .

Moreover, at time  $t = \infty$ , the capacitor is fully filled, thus  $V_c(\infty) = V_{source} = 10 \text{ V}$ .

Put the general solution:

$$V_c(t) = K_1 + K_2 e^{-\frac{t}{\tau}}$$

And substitute for  $t = 0$  and infinity, as well as the tau value. We will obtain:

$$V_c(t) = 10 - 10 e^{-6t}$$

Moreover, we know that  $V_{AB}(t) = V_{source} - V_c(t) = 10 e^{-6t}$ .

Substitute for  $t = 1$ , we will get  $V_{AB}(t) = 0.024787 V$

3)

a)

$$i) \quad V_+ = \frac{10}{25} V_2 = \frac{10}{25} (-1.5) = -0.6 V$$

From op.amp rule:  $V_- = V_+ = -0.6 V$

The current that goes to the 50kOhm resistor:  $I_- = \frac{V_1 - V_-}{50K} = \frac{2.1}{50K} = 4.2 * 10^{-5} A$

This same current flow to the 75kOhm resistor:

$$I_- = \frac{V_- - V_o}{75K}$$

$$V_o = V_- - 75k * I_-$$

$$V_o = -0.6 - 75k * 4.2 * 10^{-5} = -3.75 V$$

ii) To prevent output signal distortion,

$$|V_o| \leq 15 V$$

We know that the current that goes to the 50k resistor = The current that goes to the 75k resistor.

$$I_- = I_-$$

$$(V_1 - V_-)/50K = (V_- - V_o) / 75K$$

$$V_o = \frac{5 V_- - 3 V_1}{2}$$

$$-15 \leq \frac{5 V_- - 3 V_1}{2} \leq 15$$

$$-15 \leq \frac{5 V_- - 3 * 1.5}{2} \leq 15$$

$$-30 \leq 5 V_- - 4.5 \leq 30$$

$$-25.5 \leq 5 V_- \leq 34.5$$

$$-5.1 \leq V_- \leq 6.9$$

By voltage division rule, we know that

$$V_- = \frac{10}{25} V_2$$

$$-5.1 \leq V_- \leq 6.9$$

$$-5.1 \leq \frac{10}{25} V_2 \leq 6.9$$

$$-12.75 \leq V_2 \leq 17.25$$

b)

i)  $y_1(t)$  is not causal since it depends on input at time  $(t + 2)$ .  $y_1(t)$  is memory, because it depends on input other than  $x(t)$

$y_2(t)$  is causal.  $y_2(t)$  is memoryless.

$y_3(t)$  might be causal depending on the value of the time constant ( $t_0$ ). If  $t_0 \geq 5$ , it is causal. Otherwise, it is not causal.  $y_3(t)$  is memoryless if and only if  $t_0 = 5$   
 $y_4(t)$  is causal.  $y_4(t)$  is memory.

- ii) Yes, because memoryless system means it only depends on the current input value. While the definition of a causal system is that it depends only on the current / past input values. Thus, memoryless system is a causal system

4)

a) Yes. It is because  $y_1(t) = g(t) * f(t) = f(t) * g(t) = y_2(t)$

b)

i)  $y_o(t) = \int_{-\infty}^t x(t) dt$

$$y(t) = y_o(t) + y_o(t-3)$$

$$y(t) = \int_{-\infty}^t x(t) dt + \int_{-\infty}^{t-3} x(t-3) dt$$

We know that when  $x(t) = e^{st}$ ,  $y(t) = e^{st}H(s)$ . (Eigen function).


$$y(t) = \int_{-\infty}^t e^{st} dt + \int_{-\infty}^{t-3} e^{s(t-3)} dt$$

$$e^{st}H(s) = \frac{1}{s}e^{st} + \frac{1}{s}e^{s(t-3)}$$

$$H(s) = \frac{1}{s} + \frac{1}{s}e^{-3s}$$

$$h(t) = u(t) + u(t-3)$$

Graph:

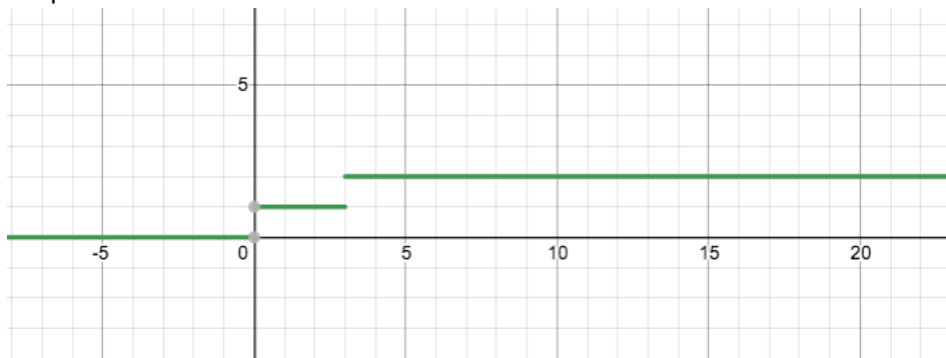

ii)  $y(t) = \int_{-\infty}^t x(t) dt + \int_{-\infty}^{t-3} x(t-3) dt$

$$y(t) = \int_{-\infty}^t \delta(t+2.5) dt + \int_{-\infty}^{t-3} \delta(t-0.5) dt$$

$$y(t) = u(t+2.5) \Big|_{-\infty}^t + u(t-0.5) \Big|_{-\infty}^{t-3}$$

$$y(t) = u(t+2.5) - u(-\infty) + u(t-3.5) - u(-\infty)$$

$$y(t) = u(t+2.5) + u(t-3.5)$$



iii) Apply Laplace transform to signal  $x(t)$

$$x(t) = 0.3 e^{-0.5t} u(t) \rightarrow X(S) = \frac{0.3}{S + 0.5}$$

$$h(t) = u(t) + u(t - 3) \rightarrow H(S) = \frac{1}{S} + \frac{e^{-3S}}{S} \dots (\text{from part 1})$$

The product of the transfer function and Laplace transform of the input signal:

$$H(S)X(S) = \frac{0.3}{S(S + 0.5)} + \frac{0.3}{S(S + 0.5)} e^{-(3S)}$$

Using partial fraction method,  $\frac{0.3}{S(S+0.5)} = \frac{A}{S} + \frac{B}{S+0.5}$

$$A = \left[ S \frac{0.3}{S(S + 0.5)} \right]_{S=0} = 0.6$$

$$B = \left[ (S + 0.5) \frac{0.3}{S(S + 0.5)} \right]_{S=-0.5} = -0.6$$

Thus,

$$H(S)X(S) = \frac{0.6}{S} - \frac{0.6}{S + 0.5} + \frac{0.6}{S} e^{-(3S)} - \frac{0.6}{S + 0.5} e^{-3S}$$

Take the inverse Laplace transform, we get:

$$y(t) = 0.6 u(t) - 0.6 e^{-0.5t} u(t) + 0.6 u(t - 3) - 0.6 e^{-0.5(t-3)} u(t - 3)$$

- c) Time based system analysis requires two steps (measuring impulse response and convolution). Frequency based needs 3 steps (Transform input signal, find transfer. Function, inverse transform of the product of the first two). However, the advantage is that there is no need to do complex integration

--End of Answers--