

Solver: Andre Sutiono

Email Address: asutiono001@e.ntu.edu.sg

1a

$$\text{Loop: } -5 \text{ V} + I_3 (1\Omega) + (I_3 + I_1)1\Omega + (I_3 + I_2)2\Omega = 0 \text{ V}$$

$$\text{Mesh: } (I_2 - I_1)(2\Omega) + (I_3 + I_2)2\Omega - 3.6\text{V} = 0 \text{ V}$$

$$I_0 = I_2 + I_3$$

$$I_1 = 1\text{A}$$

From the equations above, we can get:

$$I_3 = 0.4 \text{ V}$$

$$I_2 = 1.2 \text{ V}$$

$$I_0 = 1.6 \text{ V}$$

$$\text{Hence, } V_0 = I_0 \cdot 2\Omega = 3.2 \text{ V}$$

1b.

$$I_x = I_1 + I_2$$

$$I_2 = 4\text{A}$$


$$\text{Mesh 1: } -4 I_x + 6 I_1 + 2 I_x = 0$$

$$-4(4 + I_1) + 6 I_1 + 2(4 + I_1) = 0$$

$$12 I_1 = 8$$

$$I_1 = 2/3 \text{ A}$$

$$I_x = 4 \frac{2}{3} \text{ A}$$

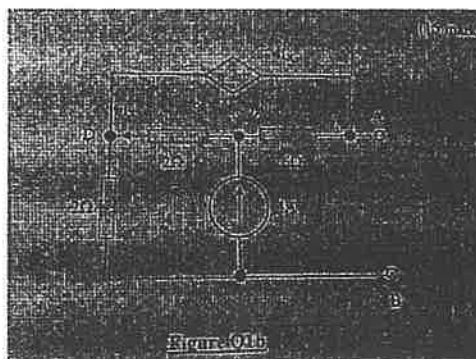

$$V_{AB} = V_{AD} + V_{DB}$$

$$= 4 I_x + 4(2)$$

$$= 26 \frac{2}{3} \text{ V}$$

$$\text{Mesh: } -v + (I_1 + I_2) 2 + I_2(2) = 0$$


$$\text{Mesh: } -v + (I_3 - I_1) 6 = 0$$

$$\text{Mesh: } -4(I_1 + I_2) + 6(I_1 - I_3) + 2(I_1 + I_2) = 0$$

Solving the above equations,

$$I_3 = 8/14 \text{ A}$$
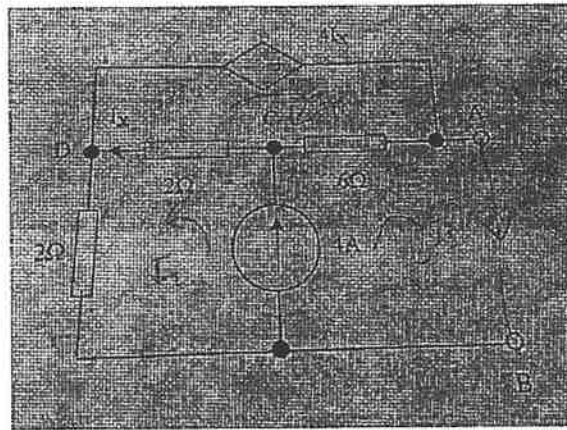
$$R_{Th} = (26 \frac{2}{3}) / (8/14) = 46 \frac{2}{3} \Omega$$



2a.i.

Using step by step approach:

$$V_c(t) = k_1 + k_2 e^{-t/\tau}$$

$$\tau = C R_{Th}$$

Short Circuiting independent voltage source and open circuiting independent current source.

$$R_{Th} = 3 // 6 = 2 \Omega$$

$$\tau = 50(10^{-6}) (2) = 10^{-4}$$

$$V_c(0^+) = k_1 + k_2 = V_c(0^-)$$

$$6 \text{ V} = I_2(6+3)$$

$$I_2 = -2/3 \text{ mA}$$

$$V_{AB} = 2/3 (6) = 4 \text{ V}$$

$$V_{CD} = 2 \text{ mA} (1 \text{ k}\Omega) = 2 \text{ V}$$

$$V_c(0^-) = V_{AB} + V_{DC} = 2 \text{ V}$$


At ∞ , capacitor acts like open circuit.

$$V_c(\infty) = k_1 = 4 \text{ V}$$

$$k_2 = 2 \text{ V} - 4 \text{ V} = -2 \text{ V}$$

$$V_c(t) = 4 - 2e^{-10000t}$$

2a.ii

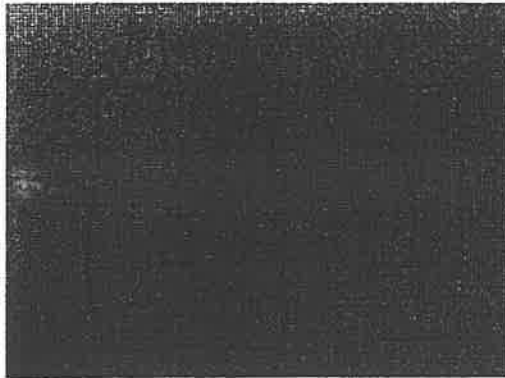

Mesh 1:

$$6 \text{ V} + (I_2(t) + I_c(t)) (6 \text{ K}\Omega) + I_2(t) (3 \text{ K}\Omega) = 0$$

Mesh 2:

$$V_c(t) + (I_2(t) + I_c(t)) (6 \text{ K}\Omega) = 0$$

Subtracting equations of mesh 2 into the one of mesh 1:

$$6 \text{ V} + I_2(t) (3 \text{ K}\Omega) - V_c(t) = 0$$

$$I_2(t) = (-6 + V_c(t)) / 3 \text{ mA}$$

$$I_2(t) = (-6 + 4 - 2e^{-10000t}) / 3 \text{ mA}$$

Using equation from mesh 2:

$$V_c(t) + (I_2(t) + I_c(t)) (6 \text{ K}\Omega) = 0$$

$$I_c(t) = (12 - 3V_c(t)) / 6 \text{ mA}$$

$$I_c(t) = (12 - 3(4 - 2e^{-10000t})) / 6 \text{ mA}$$

$$I_c(t) = e^{-10000t} \text{ mA}$$

2b.

$$R_{PQ} = ((2+2//4)+2)//2 + 2 = 3 \frac{1}{3} \text{ K}\Omega$$

$$R_{PR} = ((2+2)//4+2)//2 = 4/3 \text{ K}\Omega$$

$$R_{PS} = (((2+2)//4)+2)//2 + 1 = 2 \frac{1}{3} \text{ K}\Omega$$

$$R_{QR} = ((2+2)//4)//4 + 2 = 3 \frac{1}{3} \text{ K}\Omega$$

$$R_{QS} = (((2+2)//4)//(2+2)) + 2 + 1 = 4 \frac{1}{3} \text{ K}\Omega$$

$$R_{RS} = 1 \text{ K}\Omega$$

$$\text{Max load current} = 12 \text{ V} / (1 \text{ k}\Omega) = 12 \text{ mA}$$

3a.i.

$$y(t) = \cos(2t)x(t)$$

$$y_1(t) = \cos(2t)x_1(t)$$

$$x_2(t) = x_1(t-t_0)$$

$$y_2(t) = \cos(2t)x_2(t)$$

$$= \cos(2t) x_1(t-t_0) \text{ i}$$

$$y_1(t-t_0) = \cos(2(t-t_0)) x_1(t-t_0) \text{ ii}$$

i is not the same as ii. Therefore, $y(t)$ is time variant.

3.a.ii.

$$x_1(t) \rightarrow \cos(2t)x_1(t)$$

$$x_2(t) \rightarrow \cos(2t)x_2(t)$$

$$x_1(t) + x_2(t) \rightarrow \cos(2t)(x_1(t) + x_2(t)) \text{ i}$$

$$y_1(t) + y_2(t) = \cos(2t)(x_1(t) + x_2(t)) \text{ ii}$$

i is similar to ii. Therefore, it satisfies the additivity properties.

$$x_1(t) \rightarrow \cos(2t)x_1(t)$$


$$a x_1(t) \rightarrow a \cos(2t)x_1(t) \text{ i}$$

$$a y_1(t) = a \cos(2t)x_1(t) \text{ ii}$$

i is similar to ii. Therefore, it satisfies the homogeneity properties.

It can be concluded that $y(t)$ is linear.
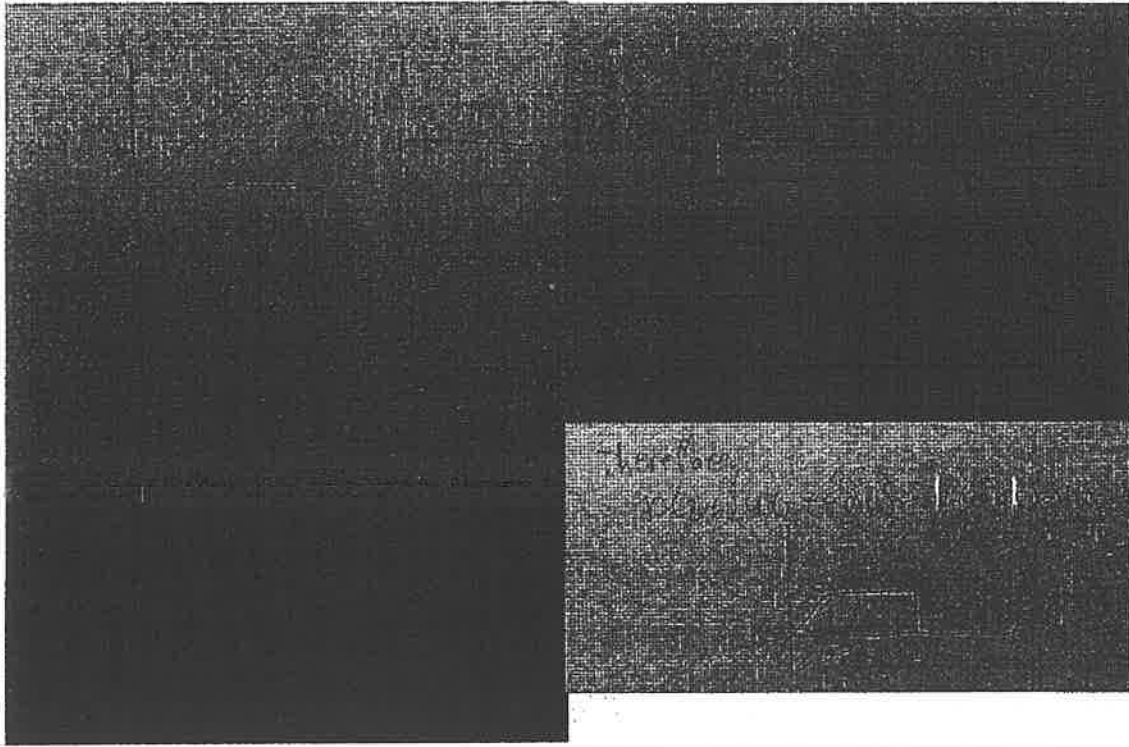
$$3b.p(t) = r(2t) u(-t + 0.5) + (u(t-0.5) - u(t-2))$$



3c.

$$y(t) = \int_{-\infty}^{\infty} x(t-T)h(T)dT$$


$$t < 0 \quad y(t) = 0$$

$$\begin{aligned} 0 < t < 0.5 \quad y(t) &= \int_0^t (2)(2)dT \\ &= \int_0^t (2)(2)dT \\ &= 4t \end{aligned}$$

$$\begin{aligned} 0.5 < t < 2 \quad y(t) &= \int_{t-0.5}^t (2)(2)dT \\ &= 2 \end{aligned}$$

$$\begin{aligned} 2 < t < 2.5 \quad y(t) &= \int_{t-0.5}^2 (2)(2)dT \\ &= 10 - 4t \end{aligned}$$

$$t > 2.5 \quad y(t) = 0$$

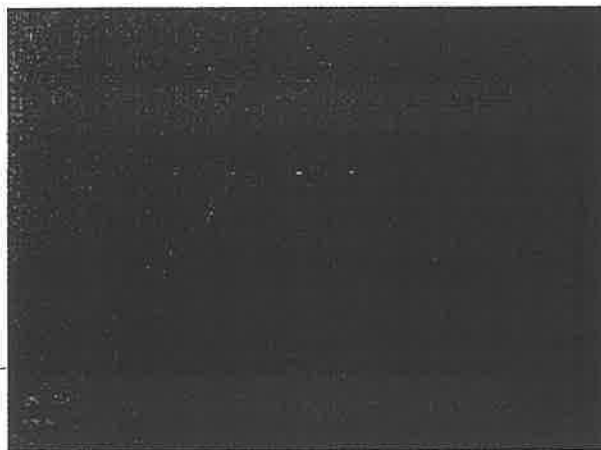

Rough Sketch is enough for the exam

4a

$$Y(t) = e^{-3t} [u(t+1) + u(t-2)]$$

$$\begin{aligned} F(Y(t)) &= \int_{-\infty}^{\infty} e^{-3t} u(t+1) e^{-j\omega t} dt + \int_{-\infty}^{\infty} e^{-3t} u(t-2) e^{-j\omega t} dt \\ &= \int_{-1}^{\infty} e^{(-3-j\omega)t} dt + \int_2^{\infty} e^{(-3-j\omega)t} dt \\ &= \frac{1}{-3-j\omega} e^{3+j\omega} + \frac{1}{-3-j\omega} e^{-(6+2j\omega)} \end{aligned}$$

4b

$$Y(s) = X(s) H(s)$$

$$X(s) = 1/s+4$$

$$H(s) = 5(1/s e^{-2s})$$

$$Y(s) = 5 \frac{e^{-2s}}{s(s+4)}$$

$$\frac{1}{s(s+4)} = \frac{A}{s} + \frac{B}{(s+4)}$$

$$A = 1/4, B = -1/4$$

$$\begin{aligned} Y(s) &= 5/4 \frac{e^{-2s}}{s} - 5/4 \frac{e^{-2s}}{s+4} \\ &= 5/4 u(t-2) - 5/4 e^{-4(t-2)} u(t-2) \end{aligned}$$

4c

$$y''(t) - y'(t) - 6y(t) = 4x(t)$$

$$s^2 y(s) - s y(s) - 6 y(s) = 4 x(s)$$

$$(s^2 - s - 6) y(s) = 4x(s)$$

$$(s^2 - s - 6) y(s) = 4(1/s e^{-s})$$

$$y(s) = \frac{4e^{-s}}{(s-3)(s+2)(s)}$$

$$\frac{4}{(s-3)(s+2)(s)} = \frac{A}{(s-3)} + \frac{B}{(s+2)} + \frac{C}{(s)}$$

$$A = -4/15, B = 2/5, C = -2/3$$

$$y(s) = \frac{-4 e^{-s}}{15(s-3)} + \frac{2 e^{-s}}{5(s+2)} - \frac{e^{-s}}{3s}$$

$$y(t) = -4/15 e^{3(t-1)} u(t-1) + 2/5 e^{-2(t-1)} u(t-1) - 2/3 u(t-1)$$

Good Luck for Your Examinations!!! Don't forget to take rest!