

Question 1

1)

a)

- i) 1011 1011
- ii) 1100 0101

b)

- i) 110 //gray code can only change one bit at a time
- ii) 101 //without having to repeat the number, the only number left is 101

c) $(a + b + c)'[(a + b c' + d')'(a' c + b' d)']'$
 $= (a' b' c')[(a + b c' + d') + (a' c + b' d)']$
 $= (a' b' c')[(a + d' + c' b + c' d)]$
 $= (a' b' c')[(a + d' + c' b + c' d)]$
 $= a' b' c' d' + a' b' c' d$
 $= a' b' c'$

d)

- i) $[(w' + x + y)(w' + x + z')(w' + y + z')(x + y + x')]'$
- ii) Refer to Fig1 below
- iii) active low output is high (asserted) when logic = 0

 


Fig1: Answers for (ii) and (iii)

Question 2

2)

a)

 


Fig2: Answers for (2a)


Source: <https://www.allaboutcircuits.com/industry-articles/an-introduction-to-schmitt-triggers-otto-schmitt/>

b) $a' c' d' + b' c' d' + a' c d + a' b c$
a,b

		00	01	11	10
c,d	00	1	1	0	1
	01	0	0	0	0
	11	1	1	0	0
	10	0	1	0	0

c)

i)

 

- ii) The output of W will be 1 when:
1. $X4 = 1$ and $Y4 = 0$
 2. $X4 = Y4$ and output from 4-bit comparator is 1

The XNOR gate compares if $X4 = Y4$

Question 3


3)

```
a) module finderrors(input[1:0] a, b, c,
                    input[1:0] sel, output[1:0] reg result);
    always @ *
    begin
        case (sel)
            2'b00: result = a;
            2'b01: result = b;
            2'b10: result = c;
            Default: result = 2'b0;
        endcase
    end
endmodule
```

```
b) module fixit(input p,q,r,z,
                output reg X,Y);
    always @ *
    begin
        if(p)
            begin
                X = q & r;
            end
        else
            begin
                X = z;
                Y = q^z;
            end
    end
end
endmodule
```

c)

i)

 

ii) //assuming inp tp be the input a, b, c with a being the MSB and c being the LSB

```

module (input[2:0] inp
        Output reg result);
always @ *
begin
case (inp)
3'b000: result = 1;
3'b001: result = 0;
3'b010: result = 1;
3'b011: result = 0;
3'b100: result = 1;
3'b101: result = 0;
3'b110: result = 0;
3'b111: result = 1;
end
endmodule


```

Question 4

4)

a)

i)

 

ii) SCSE -> 0 -> 1 -> 1 -> 0 -> 0

```

iii) module autoveh (input MOVE,
                    input reset, clk,
                    output[2:0]LOC);
parameter SCSE =3'b000, StudentGym = 3'b001,
Auditorium = 3'b011, Library = 3'b100,
InnovationCentre = 3'b010;

reg[2:0] nst, st;

assign LOC = st;
always @ (posedge clk)
begin
    if(reset)
        st <= 3'b000;
    else
        st <= nst;
end
always @ *
begin
    nst = st;
    case (st)
        SCSE:
            if(MOVE)
            begin
                nst = InnovationCentre;
                break;
            end
            else
            begin
                nst = StudentGym;
                break;
            end
        StudentGym:
            if(MOVE)
            begin
                nst = Auditorium;
                break;
            end
            else
            begin
                nst = SCSE;
                break;
            end
        Auditorium:
            if(MOVE) begin
                nst = Library;
                break;
            end
    endcase
end

```

```

        end
        else
        begin
            nst = Auditorium;
            break;
        end
    Library:
        if(MOVE) begin
            nst = Auditorium;
            break;
        end
        else begin
            nst = InnnovationCentre;
            break;
        end
    InnovationCentre:
        if(MOVE)
        begin
            nst = Library;
            break;
        end
        else begin
            nst = SCSE;
            break;
        end
    end
endcase
end
endmodule

```

```

b) module piso(input [3:0] IN, clk, LOAD,
               output out);
    reg [3:0] q;
    always @ (posedge clk)begin
        if(LOAD)
            q <= IN;
        else begin
            q[3:0] <= { q[2:0],IN[0]};
        end
    end

    assign out = q[3];

endmodule

```

== End of Answers ==

Solver: Lim Yan Jun

Email Address: ylim085@e.ntu.edu.sg